

# Analog IC Design – Xschem/Ngspice


## Lab 07

### Gm/ID Design Methodology


## PART 1: gm/ID design charts

Using ADT Device Xplore, plot the following design charts vs gm/ID for both PMOS and NMOS. Set VDS = VDD/3 and L = 0.33u,0.4u:0.4u:2u:


### 1) Gm/gds

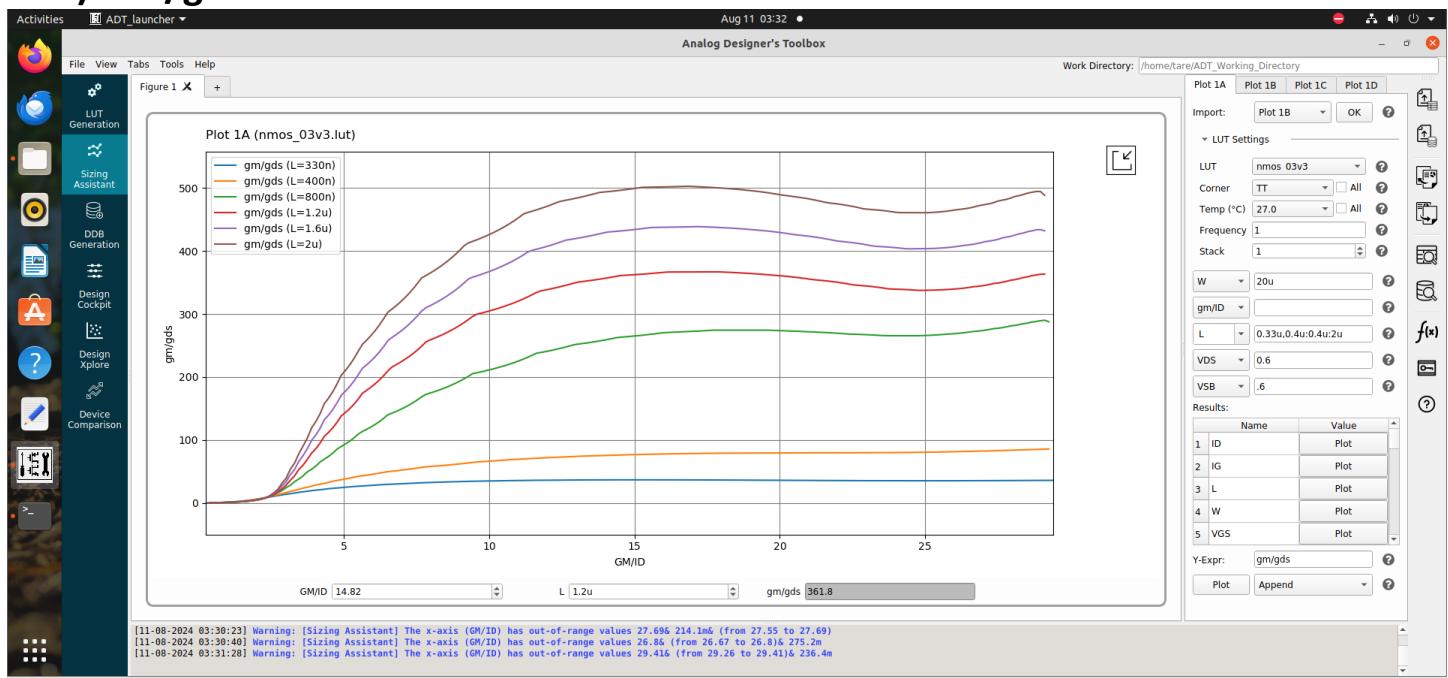


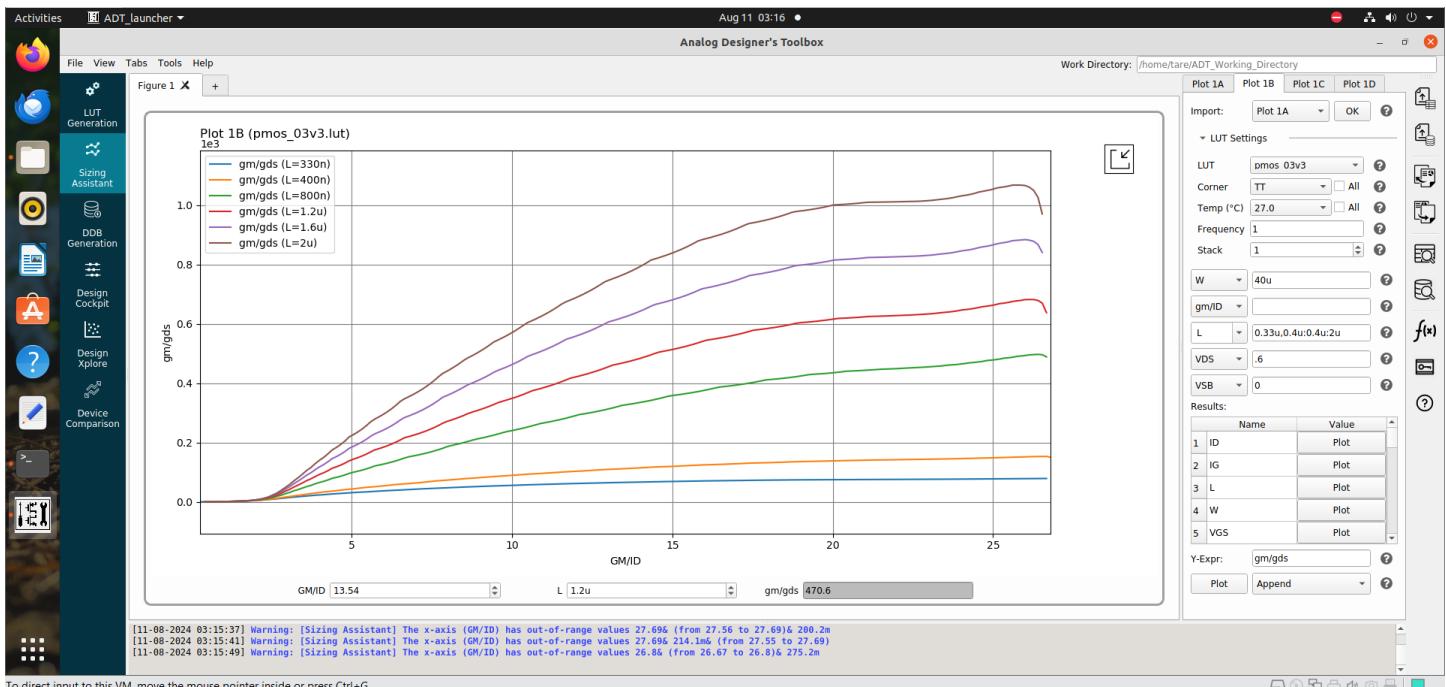To direct input to this VM, move the mouse pointer inside or press Ctrl+G.





## 2) ID/W

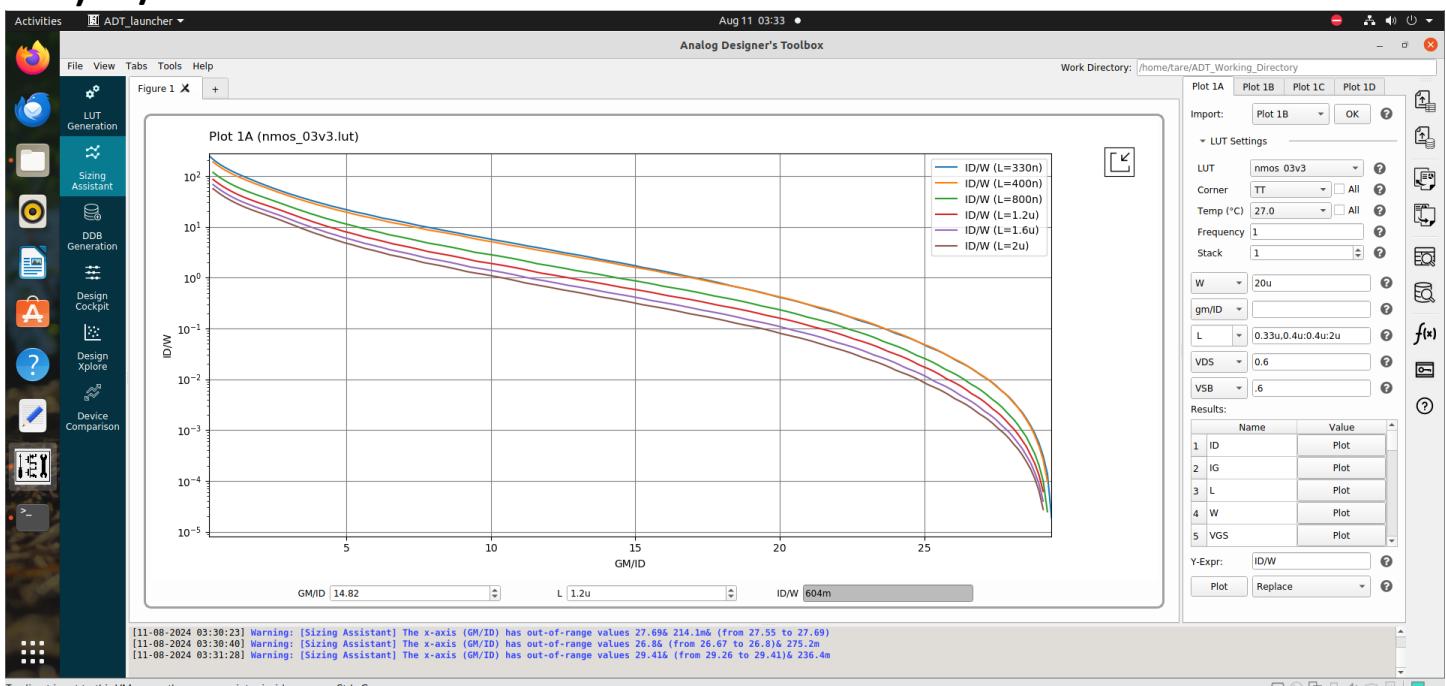

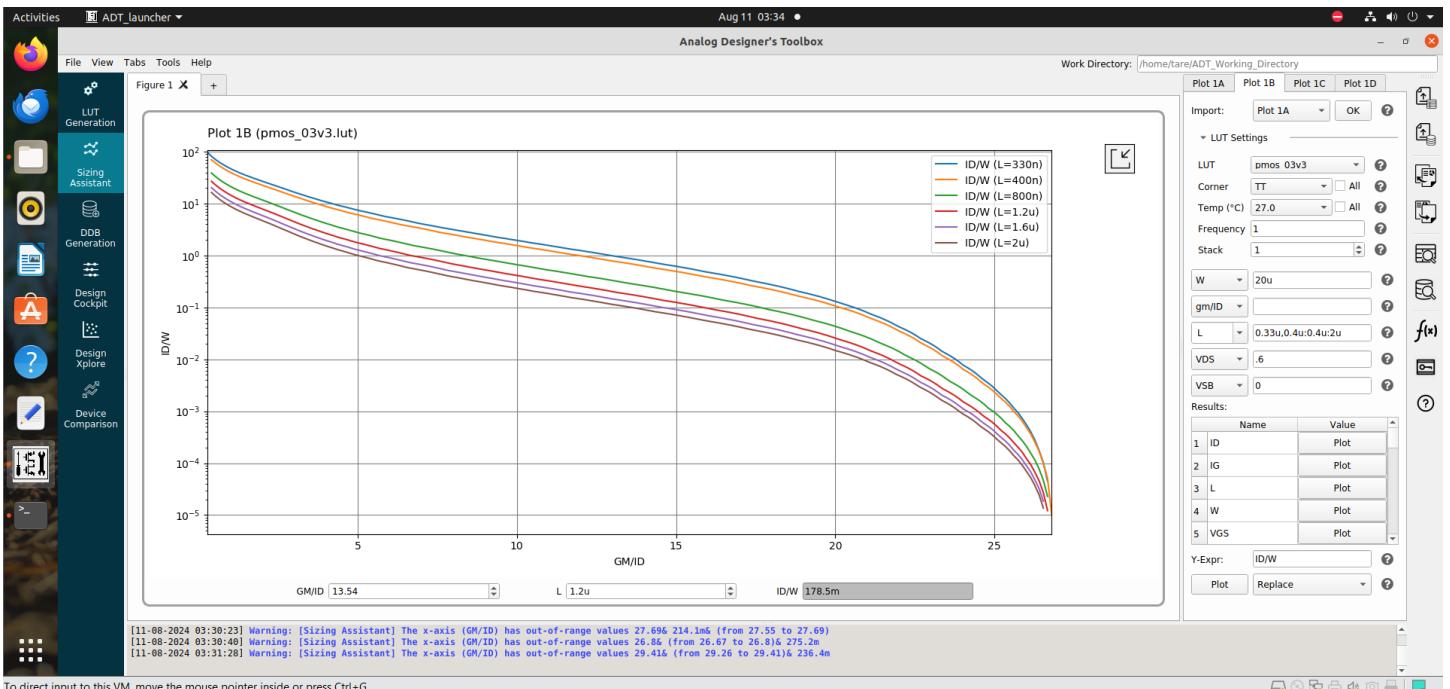



### 3) Gm/cgg (use Y expression)

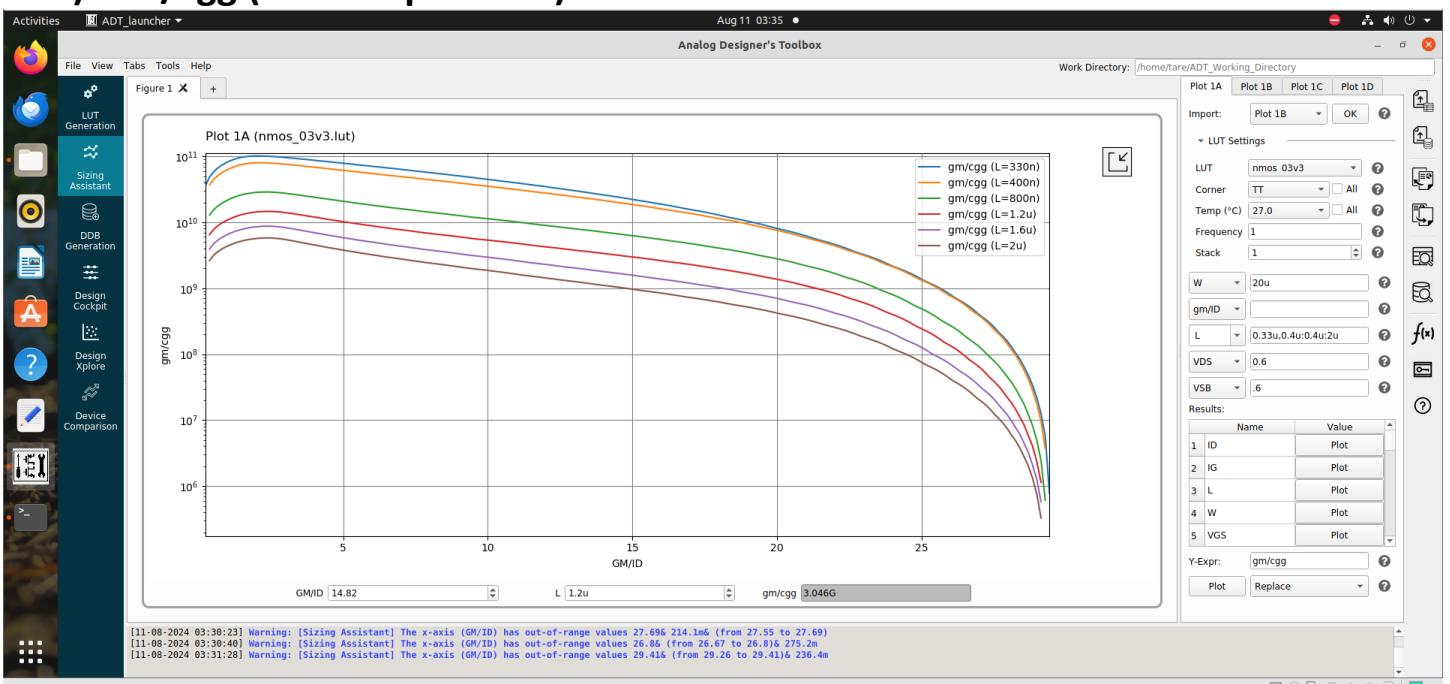

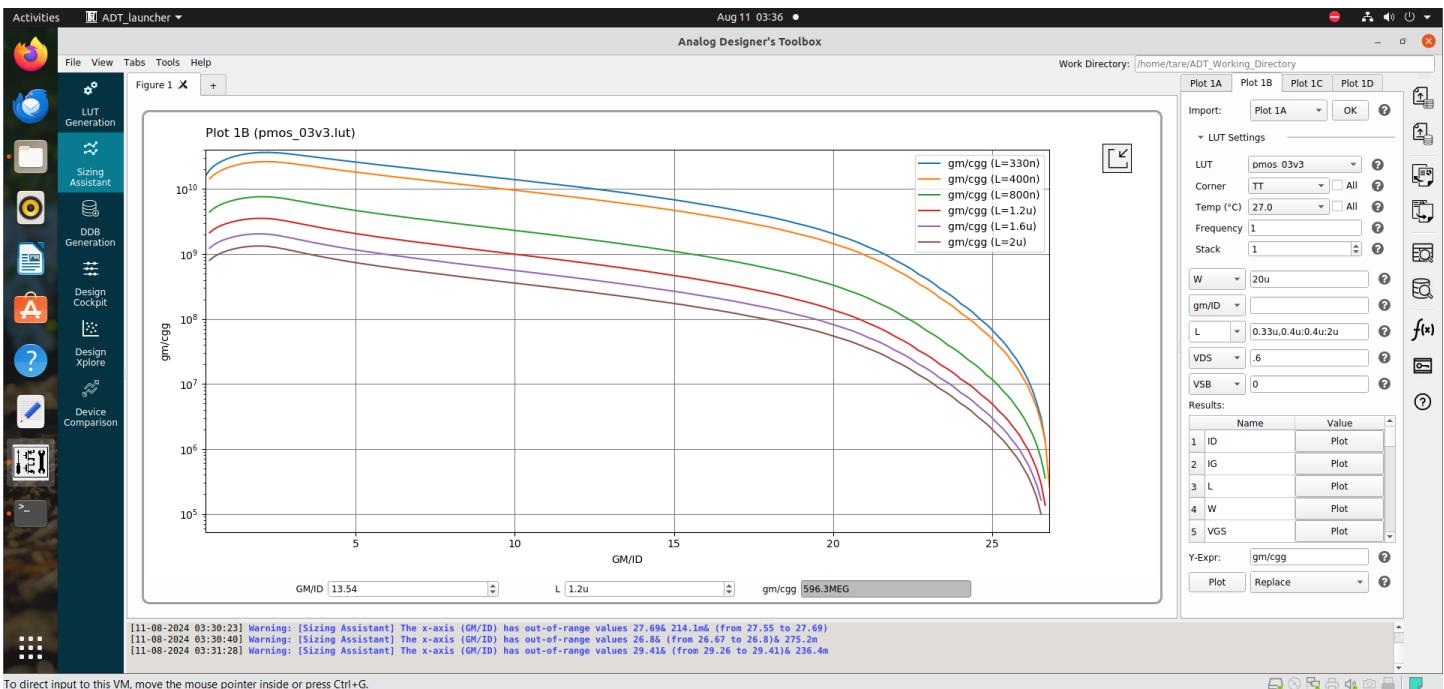

## 4) VGS

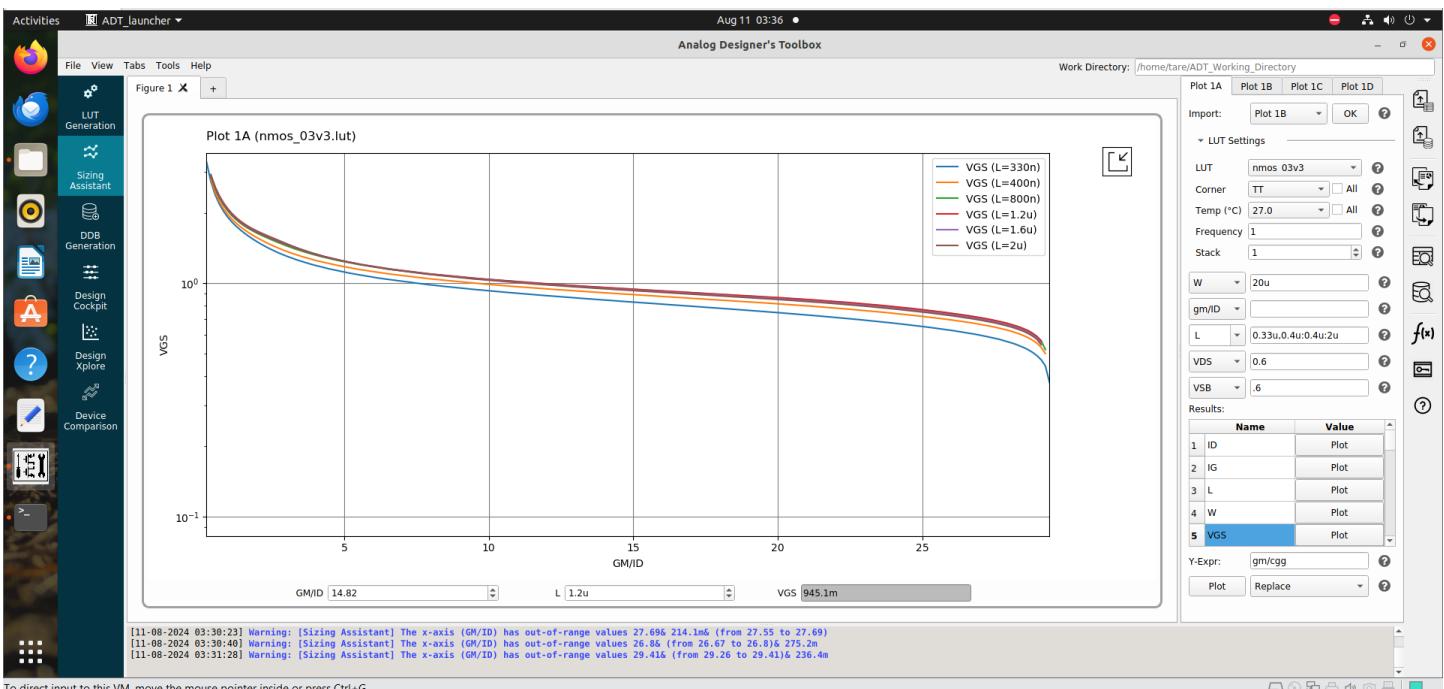

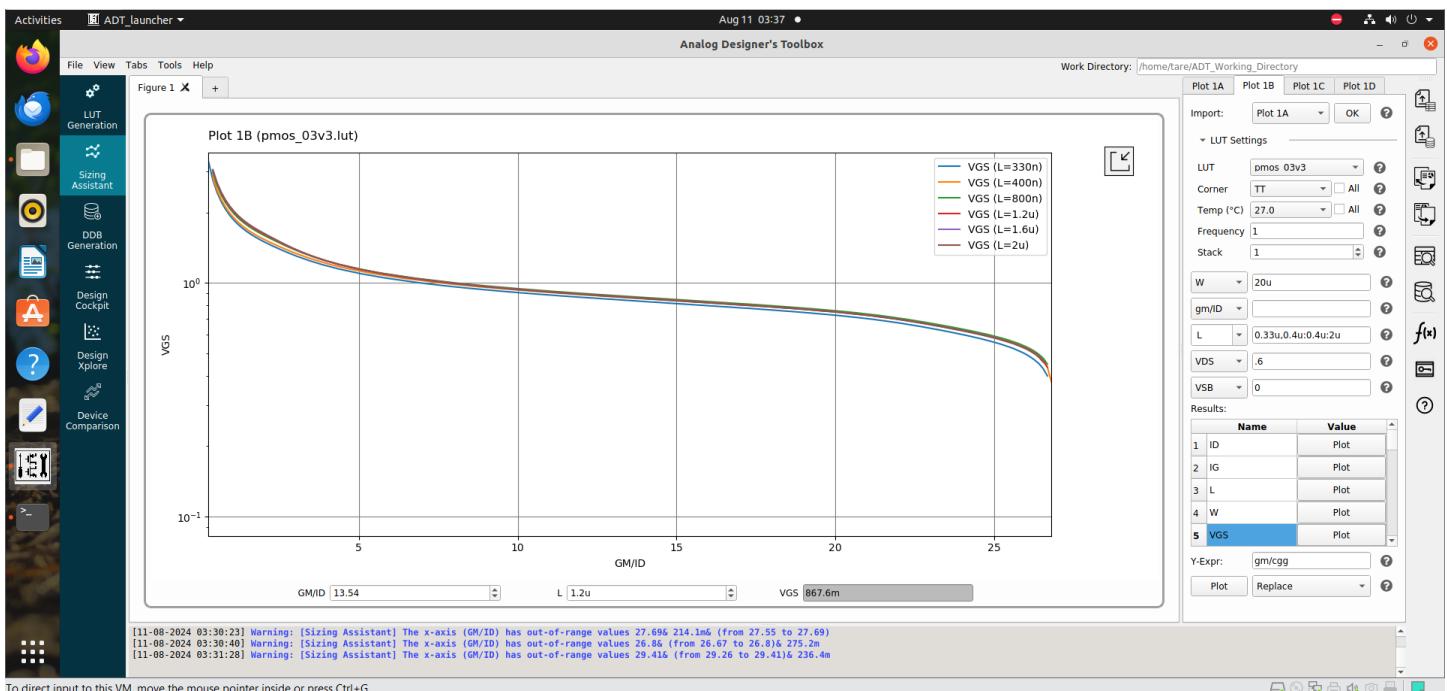

To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

## Part 2: OTA Design

**Use gm/ID methodology to design a diff input SE output operational transconductance amplifier (OTA) that achieves the following specs. Use an ideal external 10uA DC current source in your test bench (not included in the OTA current consumption spec), but design your own current mirror.**


Technology	0.13 um CMOS	0.18 um CMOS
Supply Voltage	1.2V	1.8V
Load	5pF	5pF
Open Loop DC Voltage Gain	$\geq 34\text{dB}$	$\geq 34\text{dB}$
CMRR @ DC	$\geq 74\text{dB}$	$\geq 74\text{dB}$
Phase Margin	$\geq 70^\circ$	$\geq 70^\circ$
CM input range - low	$\leq 0.6\text{V}$	$\leq 1\text{V}$
CM input range - high	$\geq 1\text{V}$	$\geq 1.5\text{V}$
GBW	$\geq 10\text{MHz}$	$\geq 10\text{MHz}$

**Report the following:**



- 1) Detailed design procedure and hand analysis. You need to make reasonable assumptions using  $gm/Id$  methodology. You need to explain why you chose the architecture that you implemented.
  - ✓ As the V<sub>ICMmax</sub> near the VDD rail and the gain is high we will choose 5T\_OTA with nmos input pair .
  - As  $GBW \approx \frac{gm_{1,2}}{2\pi * CL} = 10\text{MHz} \rightarrow gm_{1,2} = 315\mu\text{S}$  ,as we not include the parasitic capacitances at the output node we use a slightly higher  $gm_{1,2} \rightarrow gm_{1,2} = 350\mu\text{S}$ .
  - As  $Av = gm_{1,2} * (ro_2 || ro_4)$  , assume  $ro_1 = ro_2 \rightarrow Av = gm_{1,2} * \left(\frac{ro_2}{2}\right) = gm_{1,2}/2 * gds_{1,2}$
  - As  $Av >= 50 \rightarrow gm_{1,2}/gds_{1,2} >= 100$ .
  - As  $gm/ID = 10:20$  , if we assume  $ID = 20\mu\text{A} \rightarrow (gm/ID)_{1,2} = 17.5\mu\text{A}$ .
  - As the source of the input pair is floating we should include body effect into account ,so that as  $gm/ID = 17.5 \rightarrow V^* = 115\text{mV}$  , as  $VTH0 = 710\text{mV}$  ,(VTH=892mV @VSB=.6V).

So that we can estimate the value V<sub>SB</sub> , if  $V_{ICM} = 1.25\text{V}$  ,  $V^* = 115\text{mV}$  ,  $VTH \approx .8\text{V}$  ,  $VGS_{1,2} \approx 915\text{mV}$

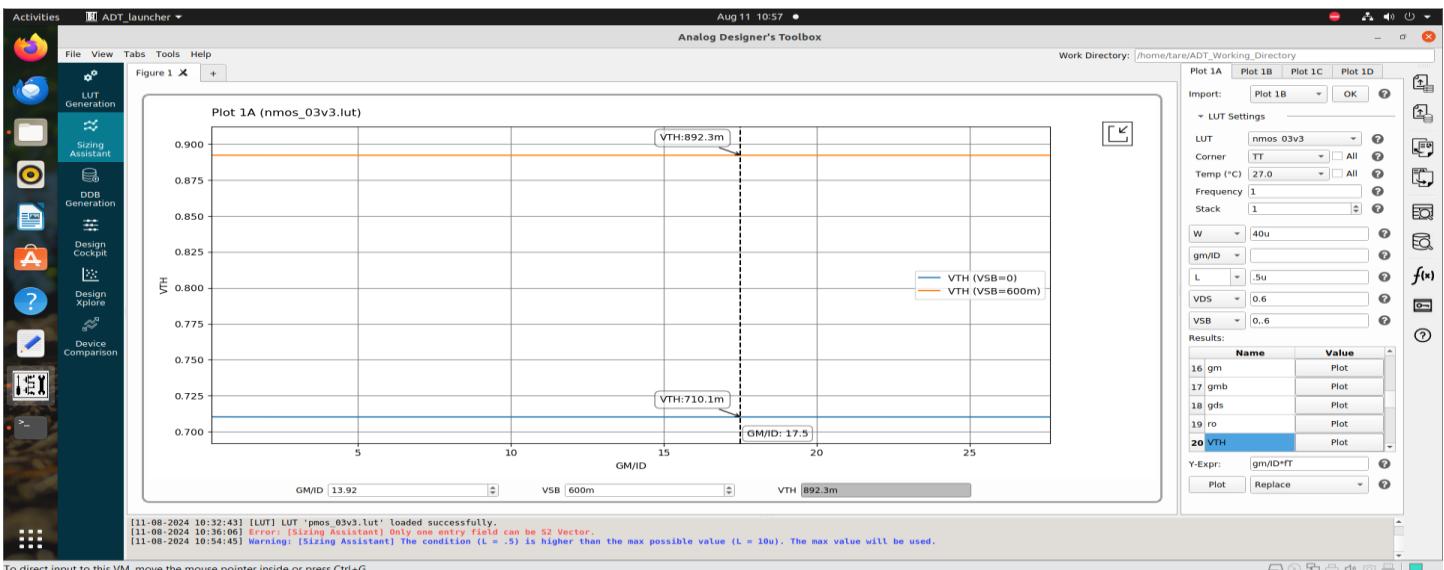
Then  $V_{SB1} = V_{DS5} = .335\text{V} = 335\text{mV}$ .



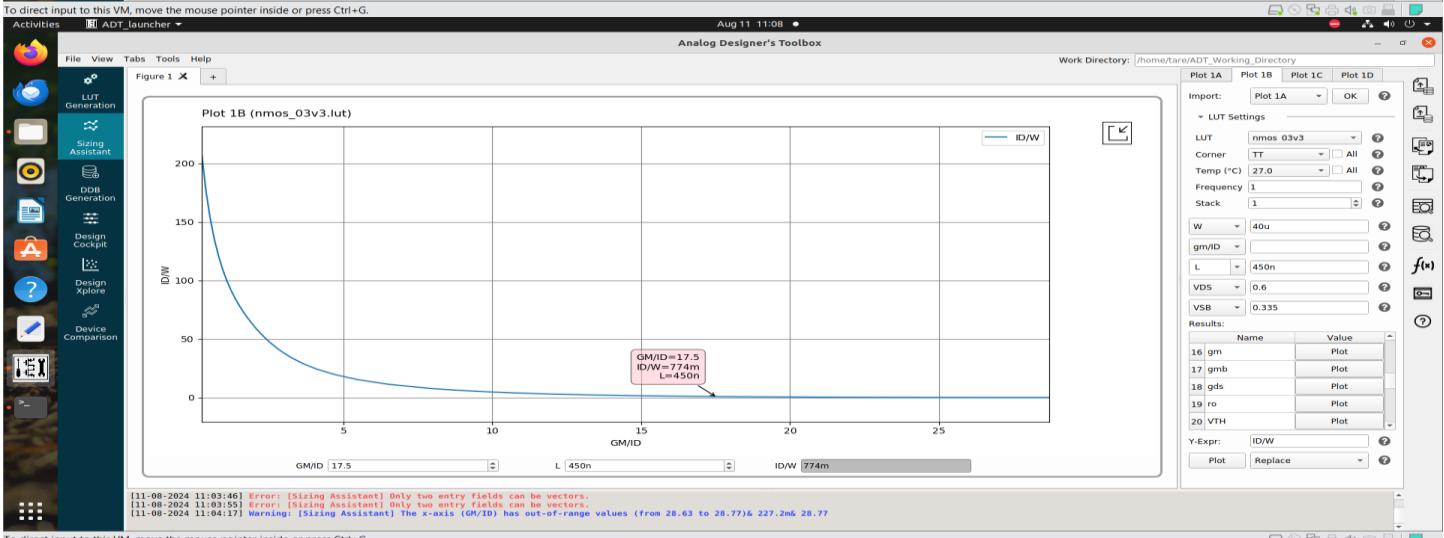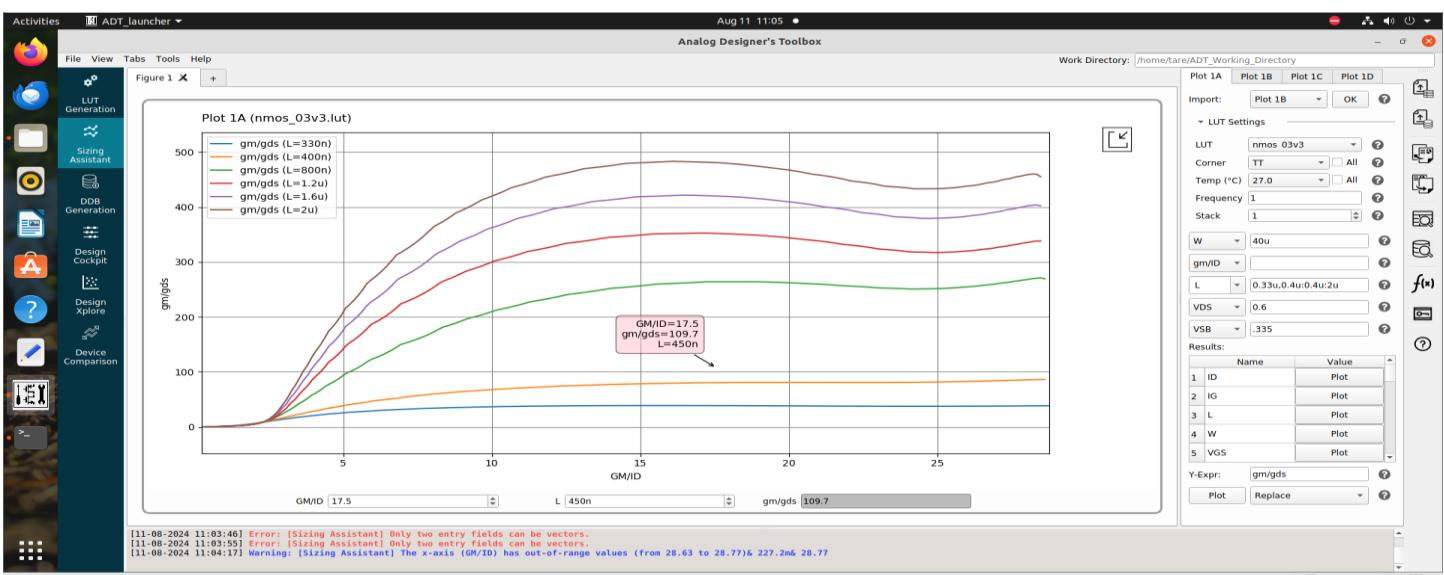- To achieve  $(gm/gds)_{1,2} \geq 100$ , then  $L_{1,2} = 450\text{nm}$ .



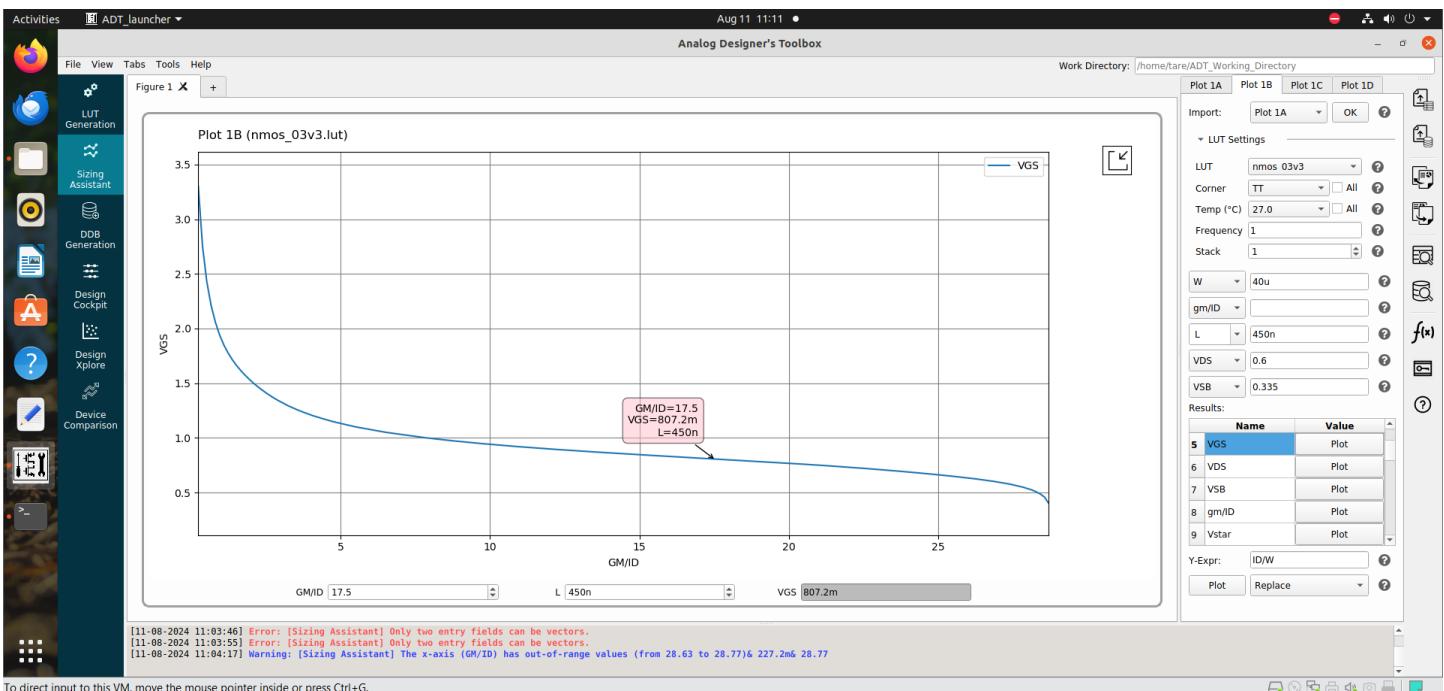- As  $ID=20\mu\text{A}$ , then  $W_{1,2}=25.84\mu\text{m}$ .




VGS<sub>1,2</sub>=807.3mV.

- As gds<sub>1,2</sub>=gds<sub>3,2</sub>=3.5uS , ID=20uA.
- As VICMmax=VDD-|VGS<sub>3,4</sub>|+(VGS<sub>1,2</sub>-V\*1,2)>=1.5 , then |VGS<sub>3,4</sub>|=<.993V.
- For the load CM to achieve small area and large ro , we choose small gm/ID=10 (strong inversion) .
- So that gm =200uS, gm/gds=>58.


So that L<sub>3,4</sub>=350nm.



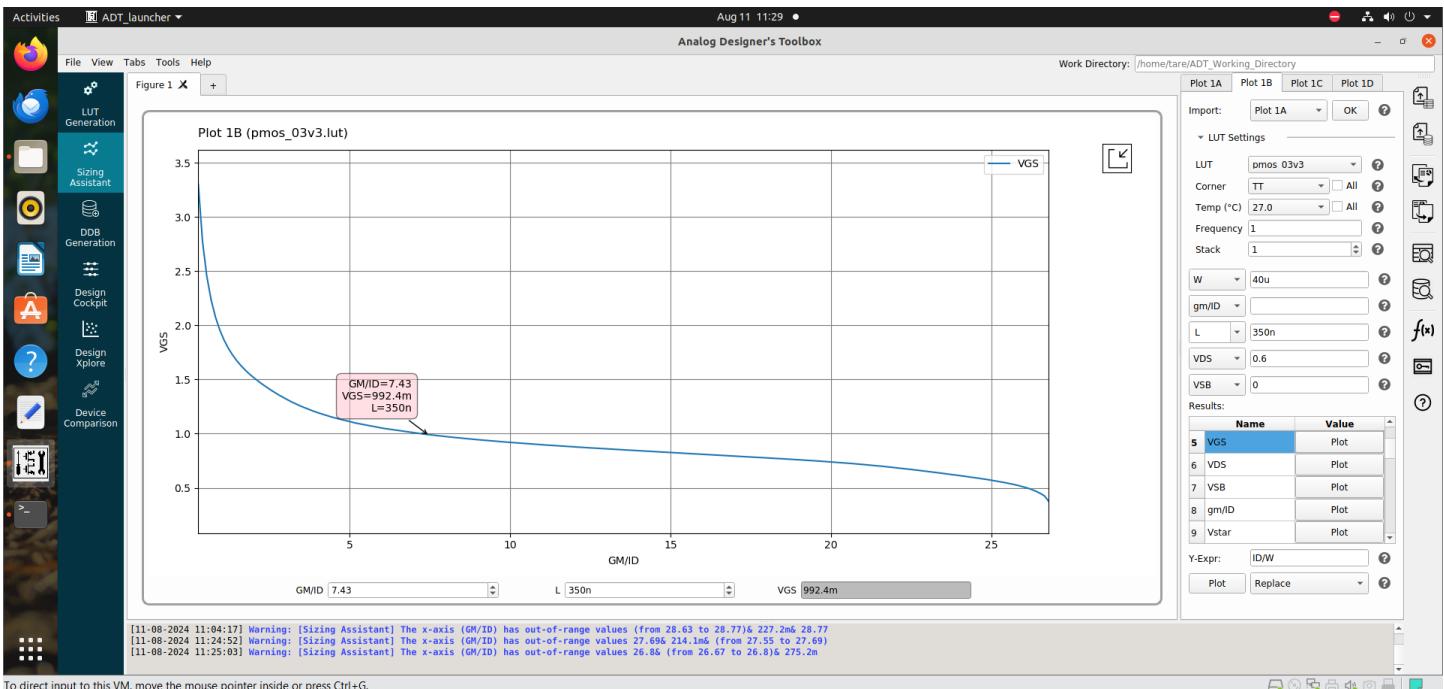

To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

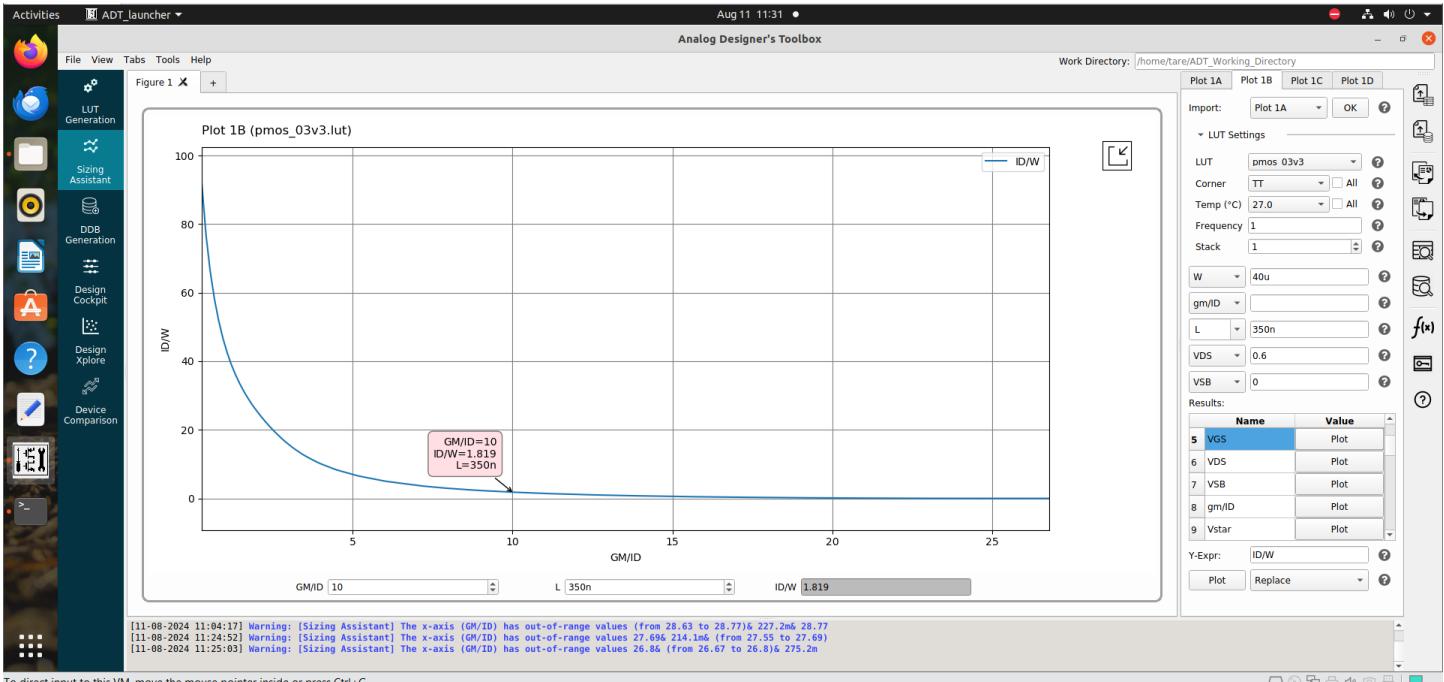- The minimum (gm/ID)=7.43 ,so that (gm/ID)=10 is good choice.





To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

As ID=20um , W3,4=11um.


- As  $A_{VCM} \approx g_{ds5}/2g_{m3,4} \leq .01$ , then  $g_{ds5} \leq 4\mu S$ .
- As  $V_{ICMmim} = V_{GS1,2} + V_{DSat5} \leq 1V$ ,  $V_{DSat5} \leq 192.8mV$  if we use  $V^*5$  as an estimate for  $V_{DSat5}$ , then  $V^* \leq 192.8mV \rightarrow (gm/ID)5 = 10.4$ .
- If we choose  $(gm/ID)5 = 12$  and  $ID = 40\mu A$ , then  $gm = 480\mu S$ ,  $(gm/gds)5 = 120$ .

Then  $L_5 = 520nm$ .

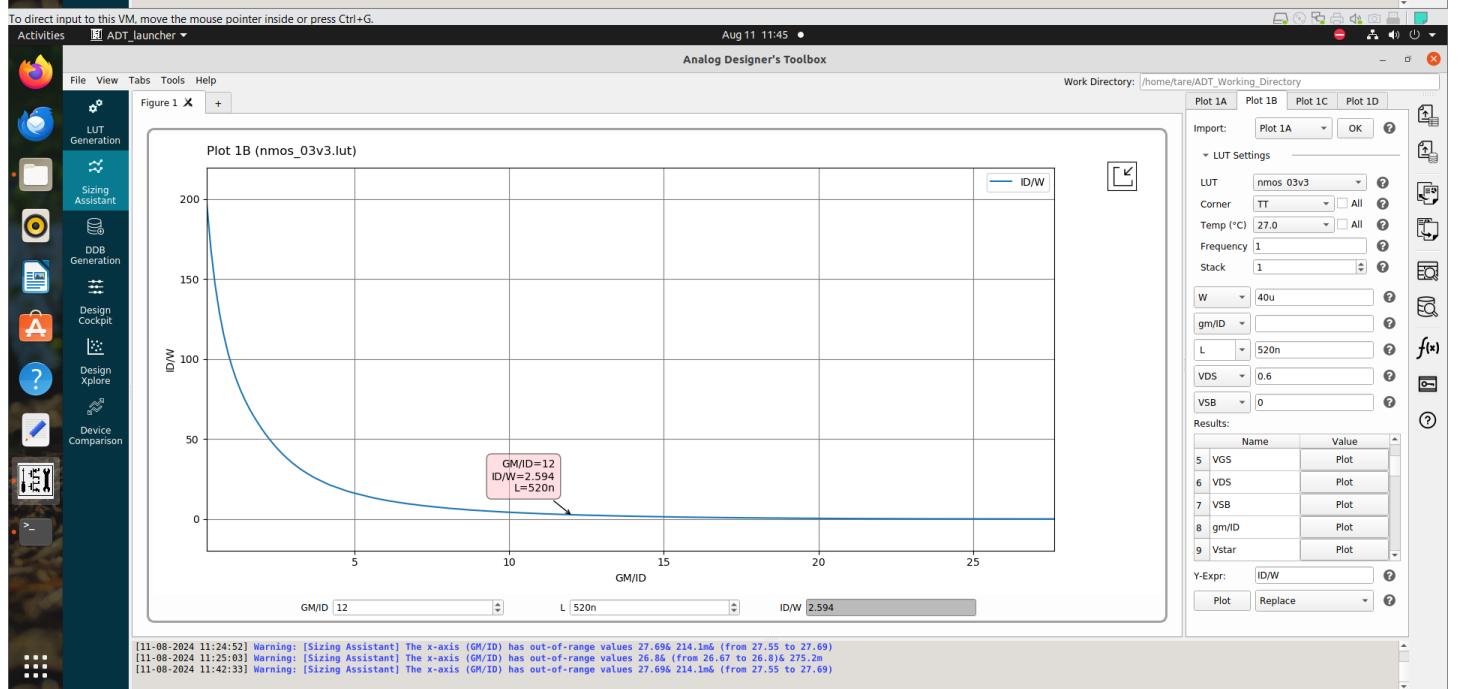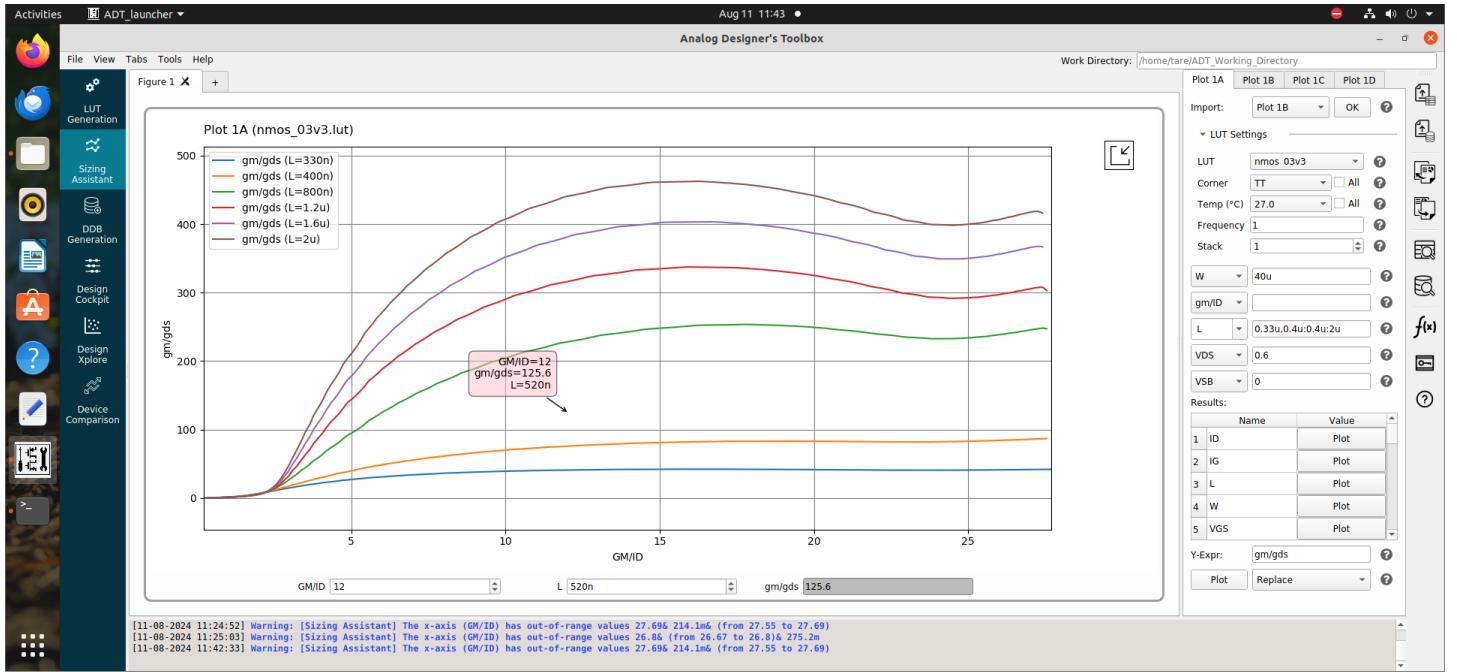

To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

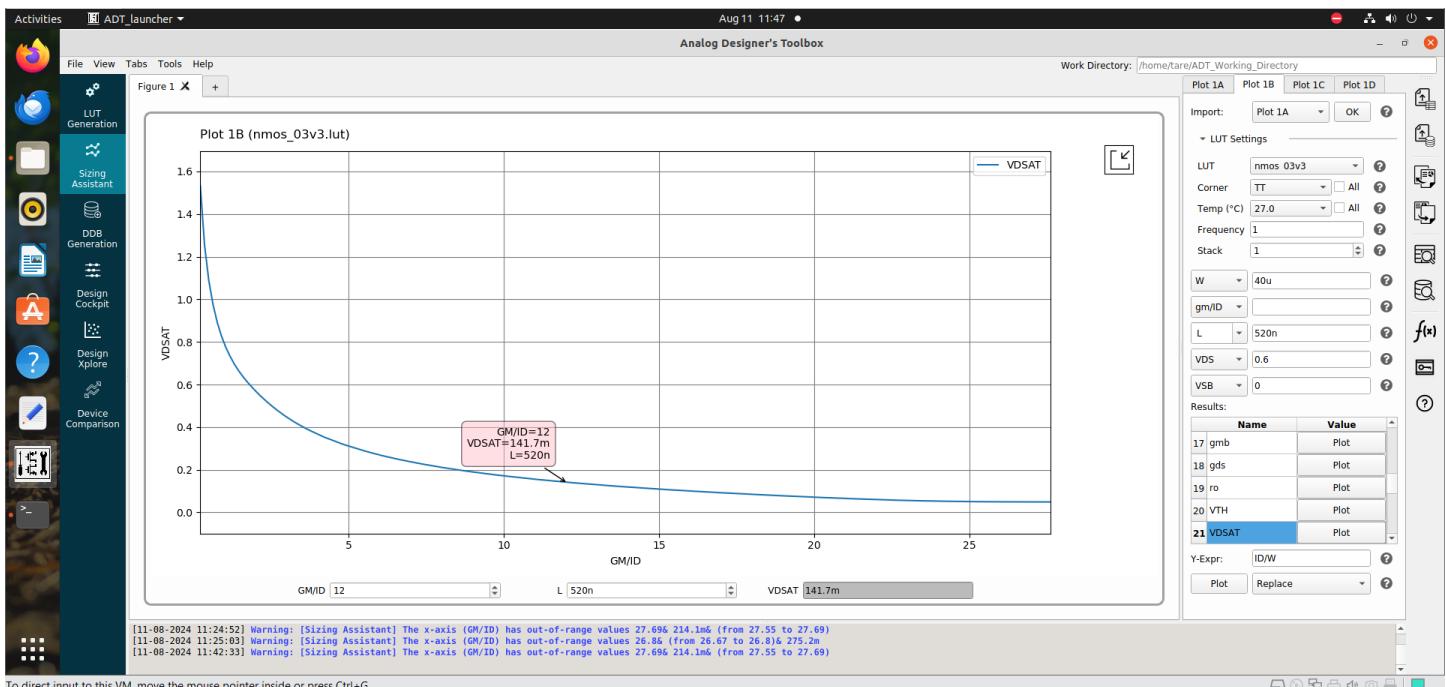As  $ID = 40\mu A$ ,  $W_5 = 15.42\mu m$ .





To direct input to this VM, move the mouse pointer inside or press Ctrl+G.


$V_{Dsat} = 141.7\text{mV}$ , which is meet the required spec.

- 2) A table showing  $W$ ,  $L$ ,  $g_m$ ,  $I_d$ ,  $g_m/I_d$ ,  $V_{dsat}$ ,  $V_{ov} = V_{gs} - V_{th}$ , and  $V^* = 2 * g_m/I_d$  of all transistors (as calculated from gm/ID curves).

	M1,2	M3,4	M5
$W$	25.84um	11um	15.42um
$L$	450nm	350nm	520nm
$G_m$	350uS	200uS	480uS
$I_d$	20uA	20uA	40uA
$G_m/I_d$	17.5S/A	10S/A	12S/A
$V_{Dsat}$	89.09mV	178.8mV	141.7mV
$V_{ov}$	1.4mV	153.9mV	94.1mV
$V^*$	115mV	200mV	167mV

## Part 3: Open - loop OTA simulation

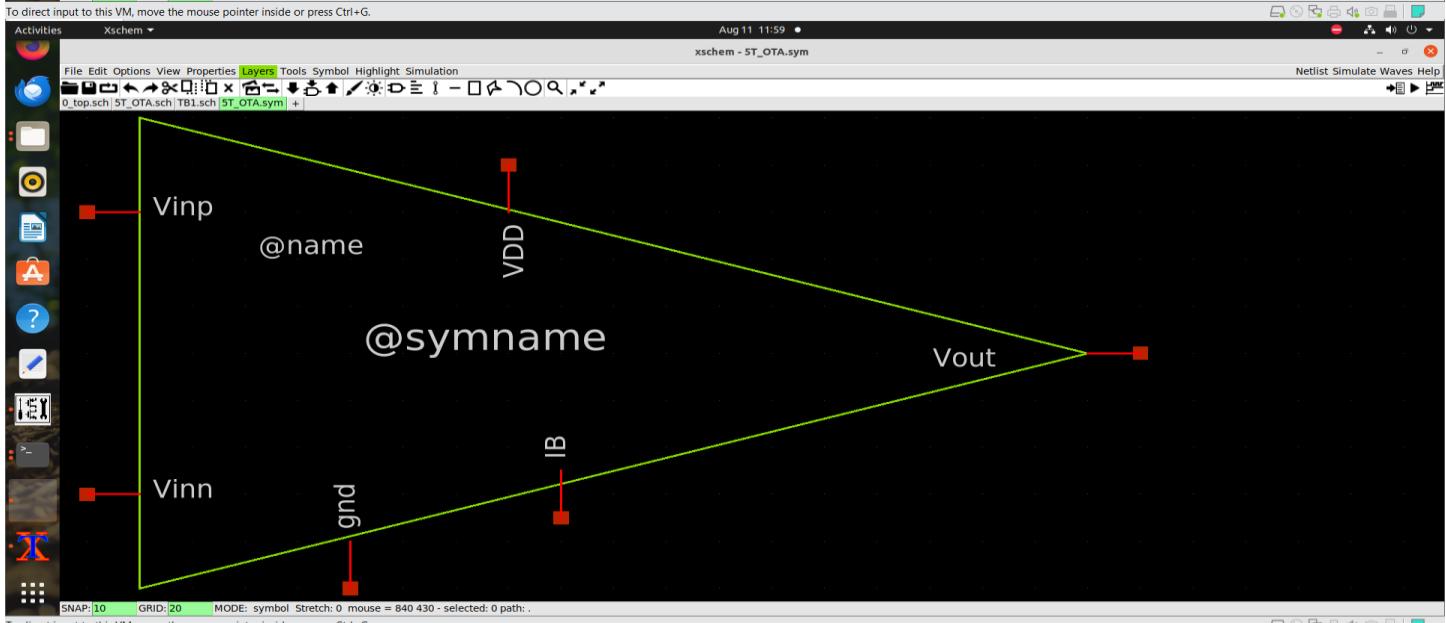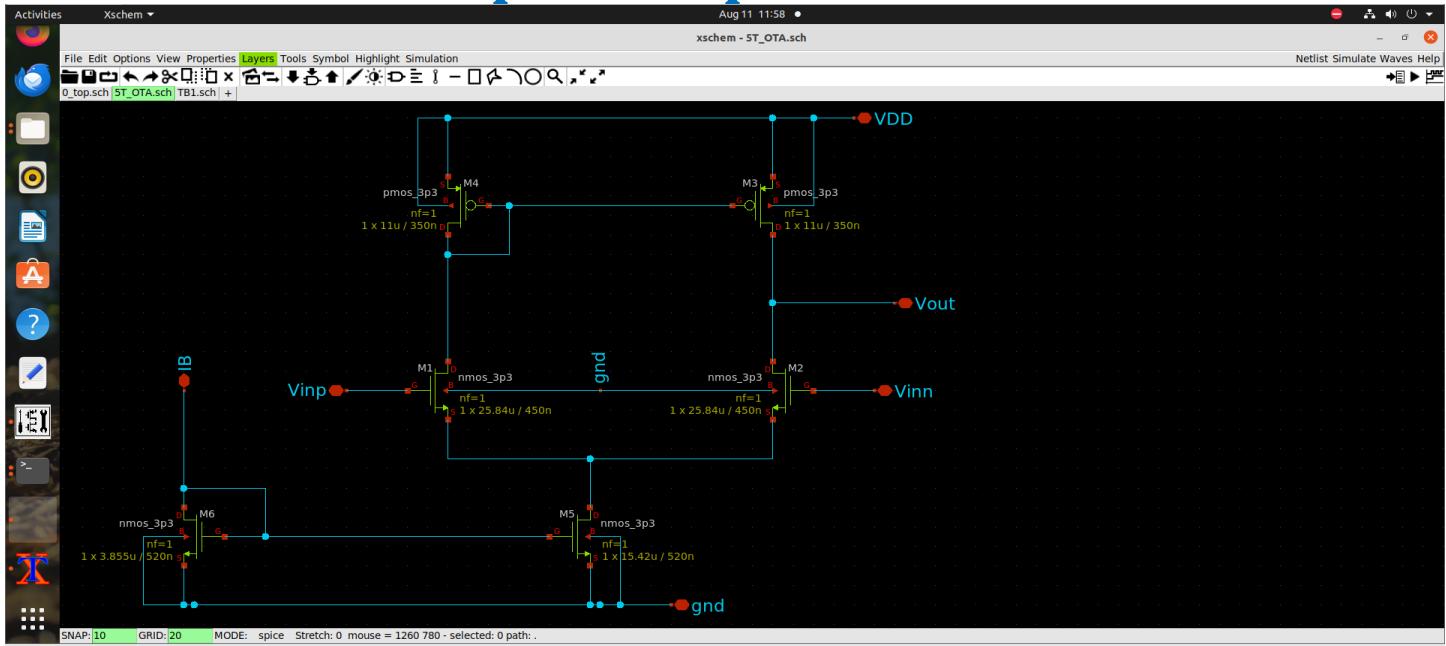

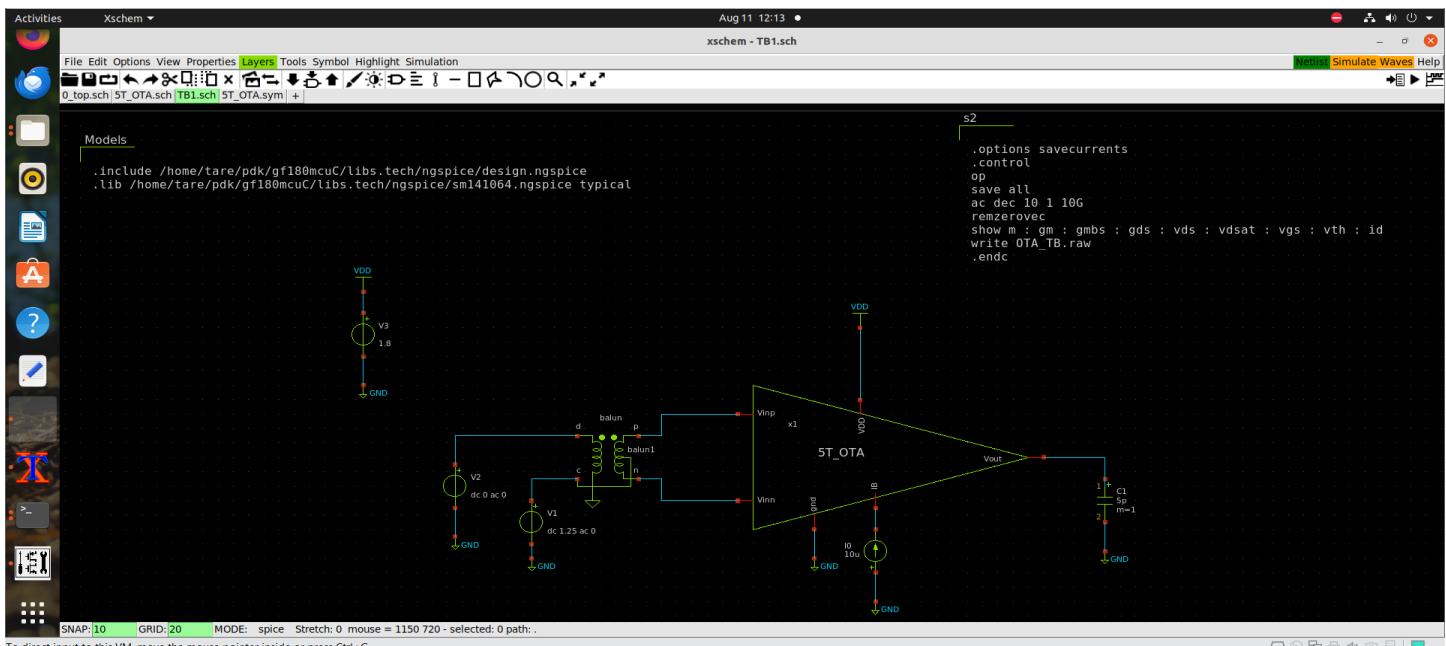

```

SNAP:10 GRID:20 MODE: spice Stretch: 0 mouse = 1150 720 - selected: 0 path: .
To direct input to this VM, move the mouse pointer inside or press Ctrl+.
TB1.spice" -a || sh

```

device	m.x1.xm6.m0	m.x1.xm6.m0	m.x1.xm4.m0
model	nmos_3p3.9	nmos_3p3.13	pmos_3p3.12
gm	0.000119943	0.000465822	0.00019885
gmb	4.31957e-05	0.000167394	7.72367e-05
gds	7.94782e-07	4.52693e-06	2.3505e-06
vds	0.80185	0.419707	0.914674
vdsat	0.141366	0.13936	0.172358
vgs	0.801854	0.801854	0.914677
vth	0.70816	0.711822	0.768212
id	1e-05	3.85733e-05	1.92866e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4

device	m.x1.xm3.m0	m.x1.xm2.m0	m.x1.xm1.m0
model	pmos_3p3.12	nmos_3p3.12	nmos_3p3.12
gm	0.00019885	0.000337041	0.000337041
gmb	7.72367e-05	9.1629e-05	9.1629e-05
gds	2.3505e-06	3.32146e-06	3.32146e-06
vds	0.914674	0.465606	0.465606
vdsat	0.172358	0.0885353	0.0885353
vgs	0.914677	0.830286	0.830286
vth	0.768212	0.831649	0.831649
id	1.92866e-05	1.92866e-05	1.92866e-05

```

binary raw file "OTA_TB.raw"
ngspice 1 -> 

```


Create a testbench as shown above. Note that IDC connection (sinking or sourcing) in the test bench may be different from the one shown above depending on the type of your input pair (PMOS/NMOS). Report the following:

## 1) Schematic of the OTA showing sizing of the transistors:

- Use VICM at the middle of the CMIR and show the operating points.
- Is the current (and gm) in the input pair exactly equal?
  - ✓ Yes ,gm of the input pair is exactly equal.
- What is DC voltage at VOUT? Why?
  - ✓ Vout=VDD-VDS3=885.33mV , which is equal to the Voltage at the mirror node, as the output node follow the mirror node.
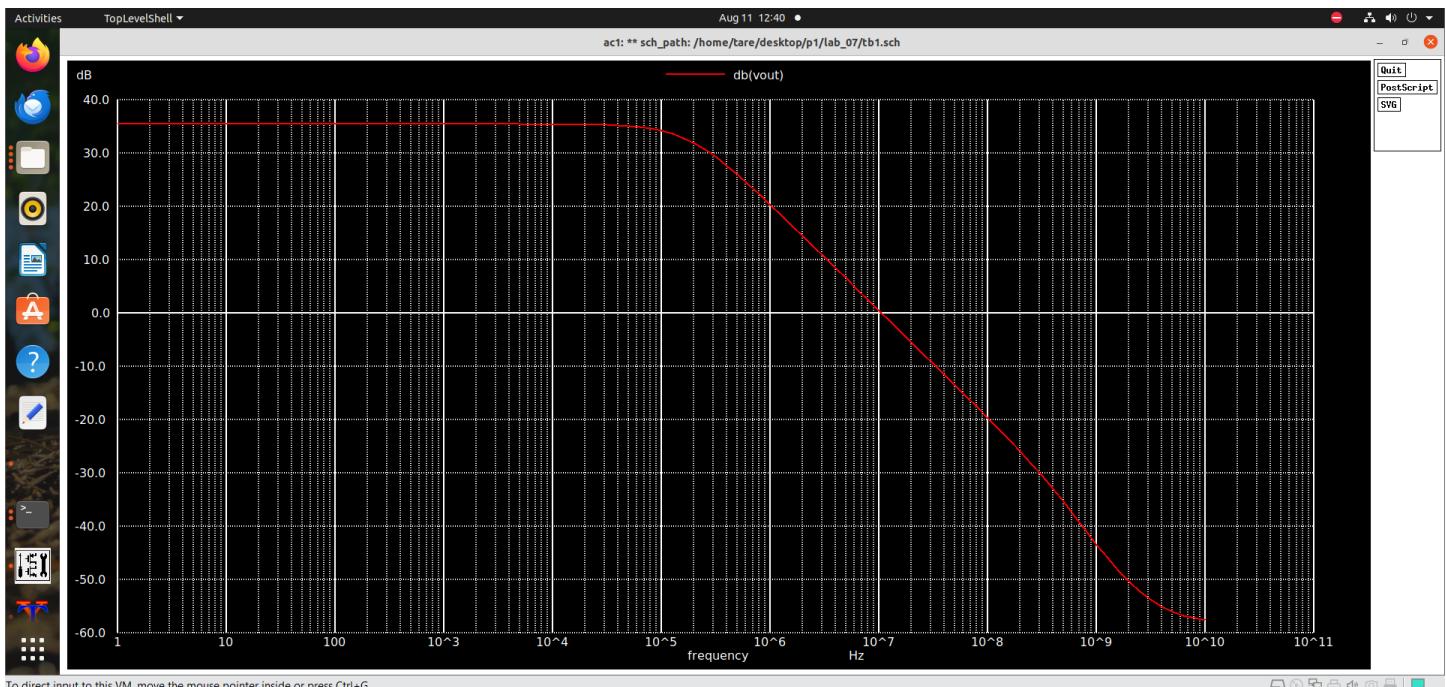
## 2) Diff small signal ccs:

- Use AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).
- Set VIDAC = 1 and VICMAC = 0.
- Use VICM at the middle of the CMIR.
- Plot diff gain (in dB) vs frequency.



To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

```
TB1.spice" -a || sh
run simulation not started
peak = 5.907288e+01 at= 2.511886e+00
f2 = 1.783044e+05
peak = 5.907288e+01
f2 = 1.783044e+05
gbw = 1.053295e+07
BSIM4v5: Berkeley Short Channel IGFET Model-4
device m_>x1_xm6_m0 m_>x1_xm5_m0 m_>x1_xm4_m0
model nmos_3p3_9 nmos_3p3_13 pmos_3p3_12
gm 0.000119943 0.000465822 0.00019885
gmbs 4.31957e-05 0.000167394 7.72367e-05
gds 7.94782e-07 4.52693e-06 2.3505e-06
vds 0.80185 0.419707 0.914674
vdsat 0.141366 0.13936 0.172358
vgs 0.801854 0.801854 0.914677
vth 0.70816 0.711822 0.768212
id 1e-05 3.85733e-05 1.92866e-05
BSIM4v5: Berkeley Short Channel IGFET Model-4
device m_>x1_xm3_m0 m_>x1_xm2_m0 m_>x1_xm1_m0
model pmos_3p3_12 nmos_3p3_12 nmos_3p3_12
gm 0.00019885 0.000337041 0.000337041
gmbs 7.72367e-05 9.1629e-05 9.1629e-05
gds 2.3505e-06 3.32146e-06 3.32146e-06
vds 0.914674 0.465606 0.465606
vdsat 0.172358 0.0885353 0.0885353
vgs 0.914677 0.830286 0.830286
vth 0.768212 0.831649 0.831649
id 1.92866e-05 1.92866e-05 1.92866e-05
binary raw file "OTA_TB.raw"
ngspice 1 -> ■
```

- Compare simulation results with hand calculations in a table.

$$Avd = \frac{gm_{1,2}}{gds_{1,2} + gds_{3,4}} = \frac{337.04\mu S}{3.32\mu S + 2.35\mu S} = 59.44V/V = 35.48db.$$


$$BW = \frac{gds_{1,2} + gds_{3,4}}{2\pi * CL} = \frac{3.32\mu S + 2.35\mu S}{2\pi * 5pF} = 180.48KHz.$$

$$GBW = \frac{gm_{1,2}}{2\pi * CL} = \frac{337.04\mu S}{2\pi * 5pF} = 10.73MHz.$$

	Hand Analysis	Simulation
Avd	59.44V/V	59.07V/V
BW	180.48KHz	178.304MHz
GBW	10.73MHz	10.53MHz
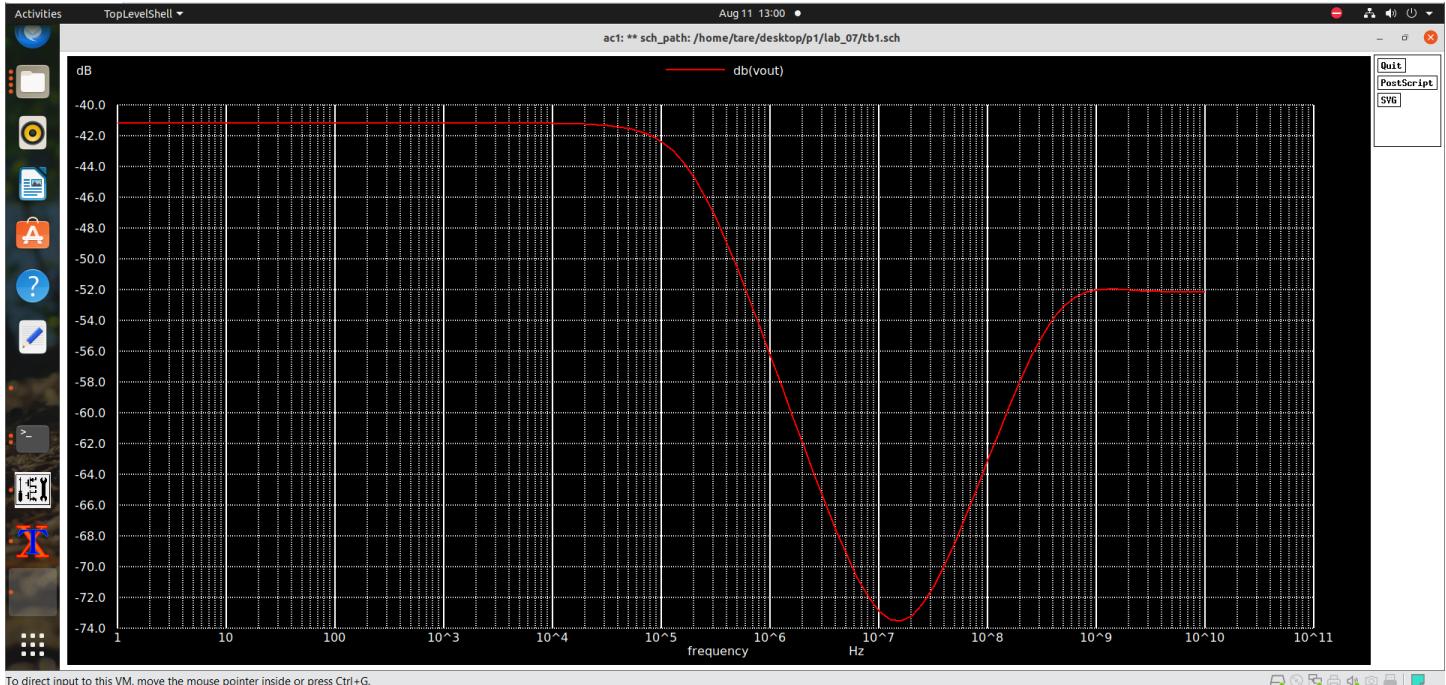
### 3) CM small signal ccs:

- Use AC analysis (1Hz:10GHz, logarithmic, 10 points/decade).
- Set VICMAC = 1 and VIDAC = 0.
- Use VICM at the middle of the CMIR.
- Plot CM gain in dB vs frequency.



To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

```
TB1.spice" -a || sh
Note: Starting dynamic gmin stepping
Trying gmin = 1.0000E-03 Note: One successful gmin step
Trying gmin = 1.0000E-04 Note: One successful gmin step
Trying gmin = 1.0000E-05 Note: One successful gmin step
Trying gmin = 1.0000E-06 Note: One successful gmin step
Trying gmin = 1.0000E-07 Note: One successful gmin step
Trying gmin = 1.0000E-08 Note: One successful gmin step
Trying gmin = 1.0000E-09 Note: One successful gmin step
Trying gmin = 1.0000E-10 Note: One successful gmin step
Trying gmin = 1.0000E-11 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Note: Dynamic gmin stepping completed

No. of Data Rows : 101
Warning: No job (tran, ac, op etc.) defined:
run simulation not started
peak = 8.730475e-03 at= 2.511886e+00
f2 = 1.783571e+05
peak = 8.730475e-03
f2 = 1.783571e+05
gbw = 1.557142e+03
binary raw file "OTA_TB.raw"
ngspice 1 -> 
```



- Compare simulation results with hand calculations in a table.

$$Av_{cm} = \frac{gds5}{2gm_{3,4}} = \frac{4.53\mu S}{2 * 198.85\mu S} = 11.39mV/V = -38.86dB.$$

	Hand Analysis	Simulation
Av <sub>cm</sub>	11.39mV/V=-38.86db	8.37mV/V=-41.18db
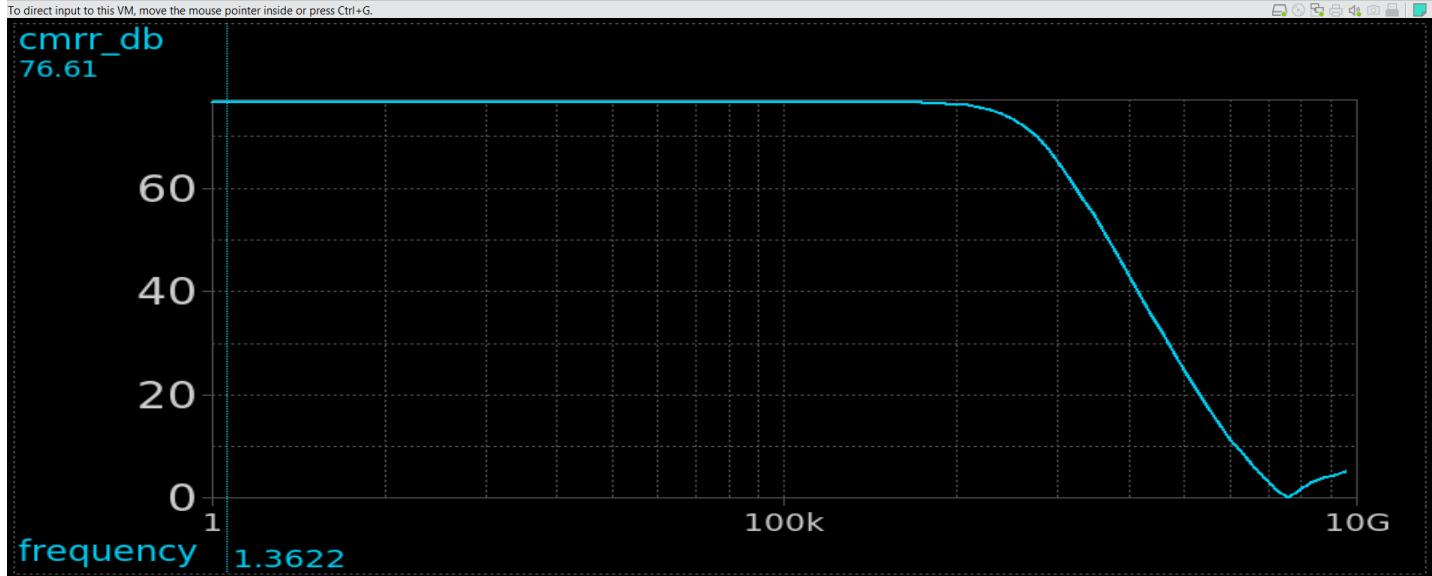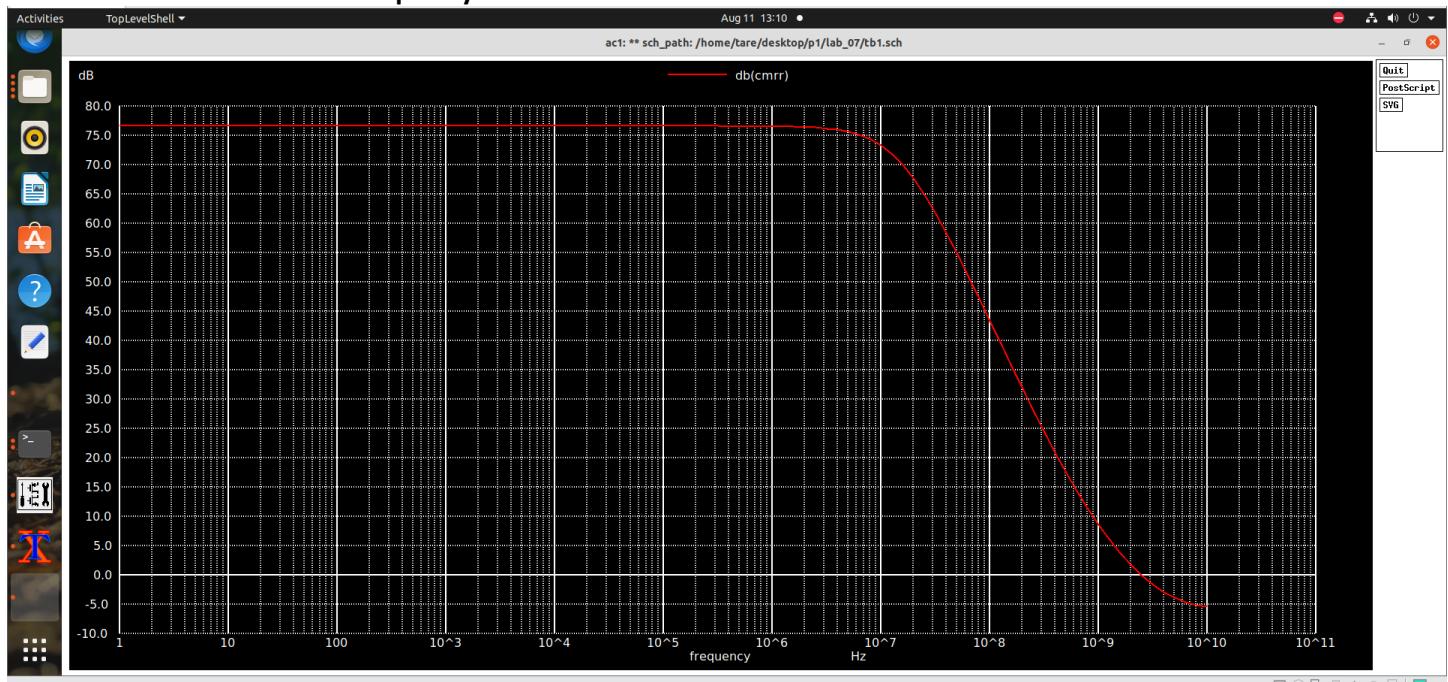
#### 4) CMRR:

- Use VICM at the middle of the CMIR.
- Plot CMRR in dB vs frequency at VICM at the middle of the CMIR.





- Compare simulation results with hand calculations in a table.


	Hand Analysis	Simulation
CMRR	5.22KV/V=74.35db	76.61db
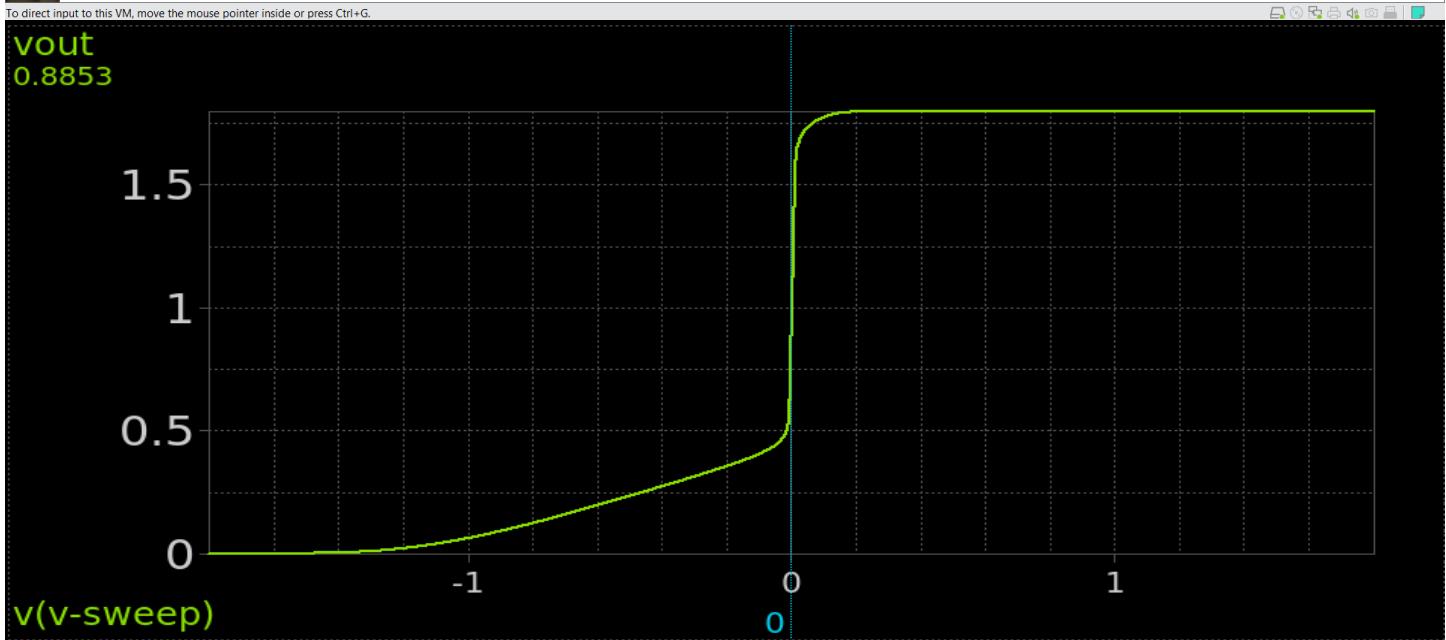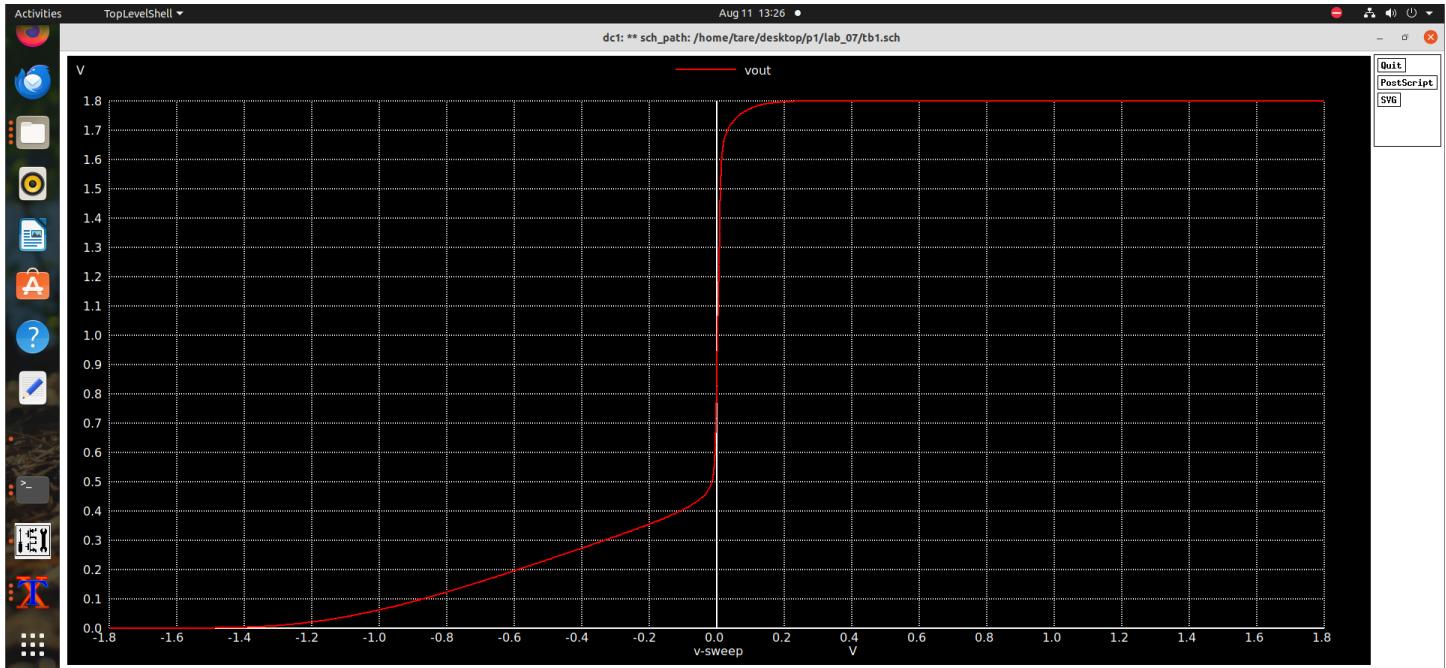
## 5) Diff large signal ccs:


- Use VICM at the middle of the CMIR.
- Use DC sweep (not parametric sweep) VID = -VDD:1m: VDD. You must use a small step (1mV) because the gain region is very small (steep slope).
- Plot VOUT vs VID.



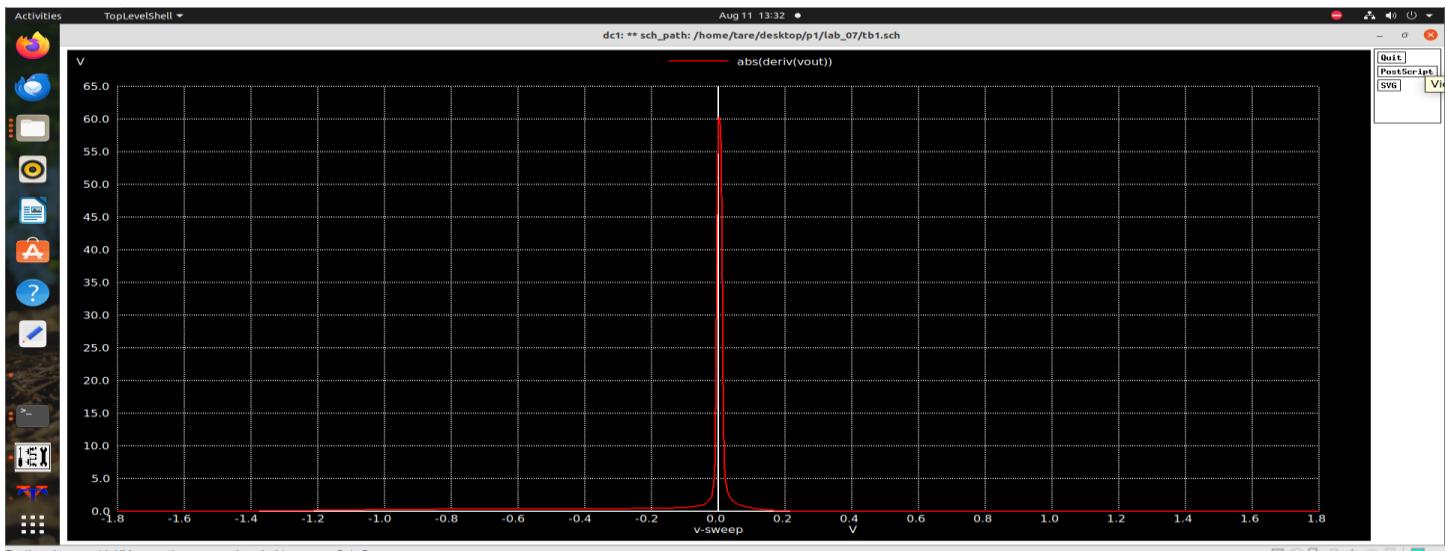- From the plot, what is the value of Vout at VID = 0? Why?
  - ✓ Vout=.8853V , at VID=0 no differential signal only CM ,so that Vout follow mirror node in the CM so that Vout=885.3mV which is equal to VF.
- Plot the derivative of VOUT vs VID. Compare the peak with Avd.



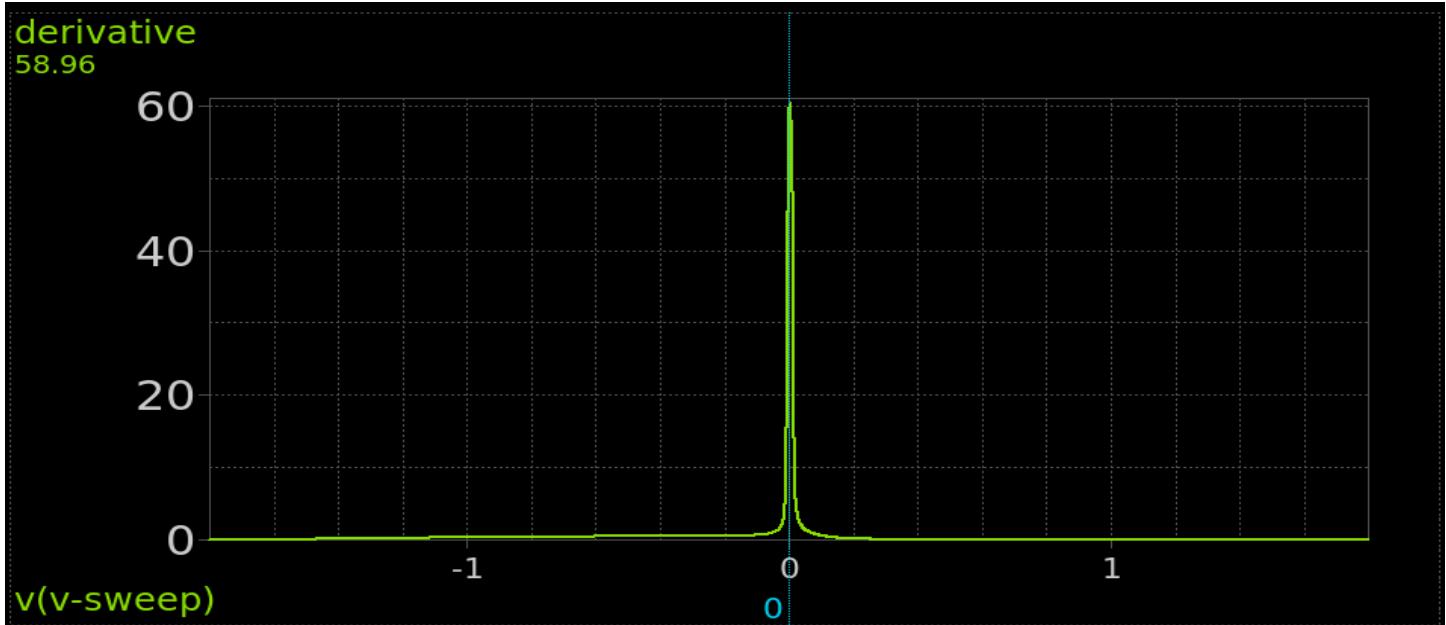To direct input to this VM, move the mouse pointer inside or press Ctrl+G.




```
TB1.spice" -a || sh
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Note: Starting dynamic gmin stepping
Trying gmin = 1.0000E-03 Note: One successful gmin step
Trying gmin = 1.0000E-04 Note: One successful gmin step
Trying gmin = 1.0000E-05 Note: One successful gmin step
Trying gmin = 1.0000E-06 Note: One successful gmin step
Trying gmin = 1.0000E-07 Note: One successful gmin step
Trying gmin = 1.0000E-08 Note: One successful gmin step
Trying gmin = 1.0000E-09 Note: One successful gmin step
Trying gmin = 1.0000E-10 Note: One successful gmin step
Trying gmin = 1.0000E-11 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Trying gmin = 1.0000E-13 Note: One successful gmin step
Note: Dynamic gmin stepping completed
Reference value : 0.00000e+00
No. of Data Rows : 1
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Reference value : 6.04000e-01
No. of Data Rows : 3601
peak = 6.030701e+01 at= 2.000000e-03
binary raw file "OTA_TB.raw"
ngspice 1 -> ■
```

Deriv(Vout)max=60.307 , which is almost equal to Avd.

## PART 4: Closed-Loop OTA Simulation

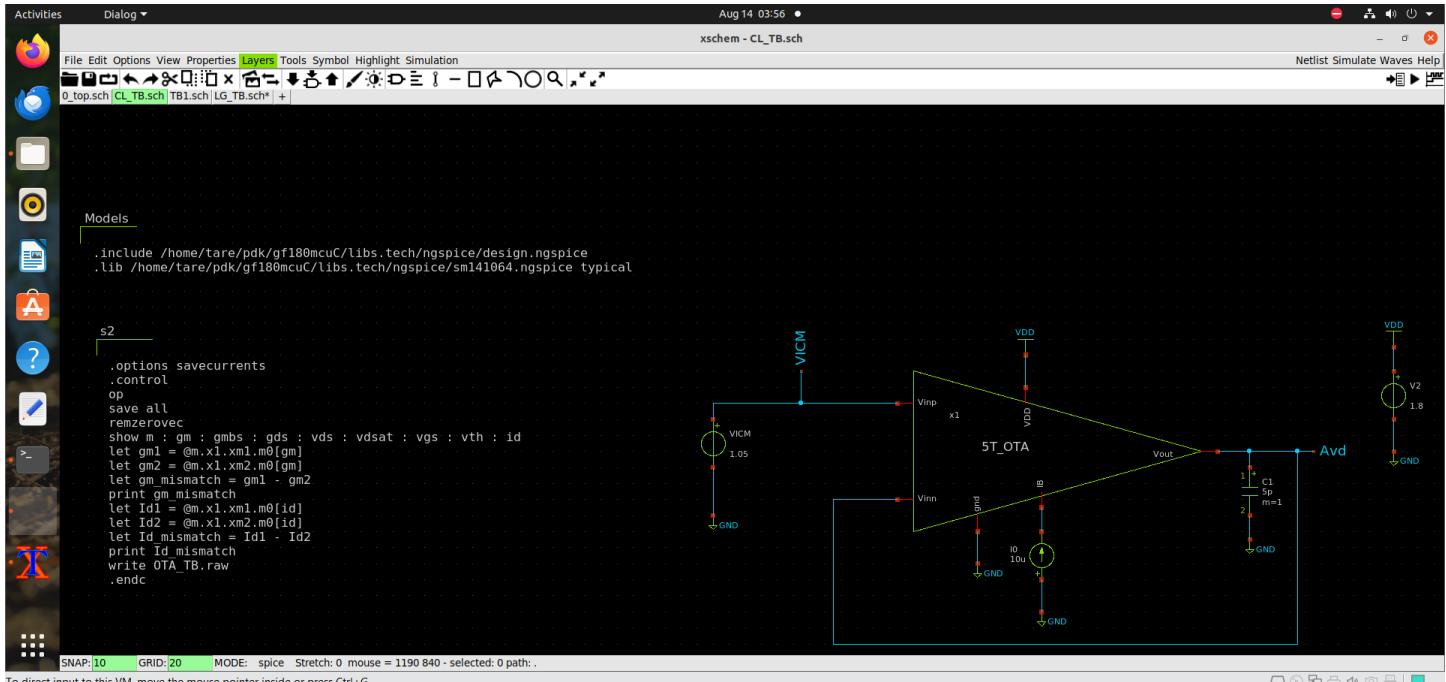- 1) Create schematic of the OTA showing current and  $gm$  operating point. Use  $VINCM = CMIRlow + 50 \text{ mV}$ .



To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

```

CL_TB.spice" -a || sh
No. of Data Rows : 1
BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m_x1xm6.m0      m_x1xm5.m0      m_x1xm4.m0
model      nmos_3p3.9      nmos_3p3.13      pmos_3p3.12
gm        0.000119943     0.000453647    0.000197271
gmb       4.31957e-05     0.000163038    7.66183e-05
gds       7.94782e-07     8.50926e-06    2.32602e-06
vds        0.80185        0.265414       0.913364
vdsat      0.141366       0.139265       0.171345
vgs        0.801854       0.801854       0.913366
vth        0.70816        0.711963       0.768219
id         1e-05          3.76616e-05    1.9024e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device      m_x1xm3.m0      m_x1xm2.m0      m_x1xm1.m0
model      pmos_3p3.12      nmos_3p3.12      nmos_3p3.12
gm        0.000193978     0.00032844    0.000333799
gmb       7.54305e-05     9.59695e-05    9.75479e-05
gds       2.4888e-06      2.72823e-06    2.95071e-06
vds        0.752538       0.782036       0.62121
vdsat      0.170716       0.0858852     0.0868541
vgs        0.913366       0.782037       0.784579
vth        0.769038       0.788058       0.788464
id         1.86376e-05     1.86376e-05    1.9024e-05

gm_mismatch = 5.358392e-06
id_mismatch = 3.863634e-07
binary raw file "OTA_TB.raw"
ngspice 1 -> 

```

- Is the current (and  $gm$ ) in the input pair exactly equal? Why?
  - ✓ no gm and ID not exactly equal, as the amplifier has a finite Loop gain then there is some error between the two input this small error generate a small differential signal between the two inputs which cause the error in gm and id .
- Calculate the mismatch in  $Id$  and  $gm$ .


$$\text{As } LG \approx 59.44, \text{ then } Verr = \frac{V_{in} - 1.05}{1 + LG} = \frac{1.25 - 1.05}{1 + 59.44} = 3.33 \text{ mV.}$$

$$\Delta ID \approx 386.4 \text{nA.}$$


$$\Delta gm \approx 5.36 \mu\text{S.}$$
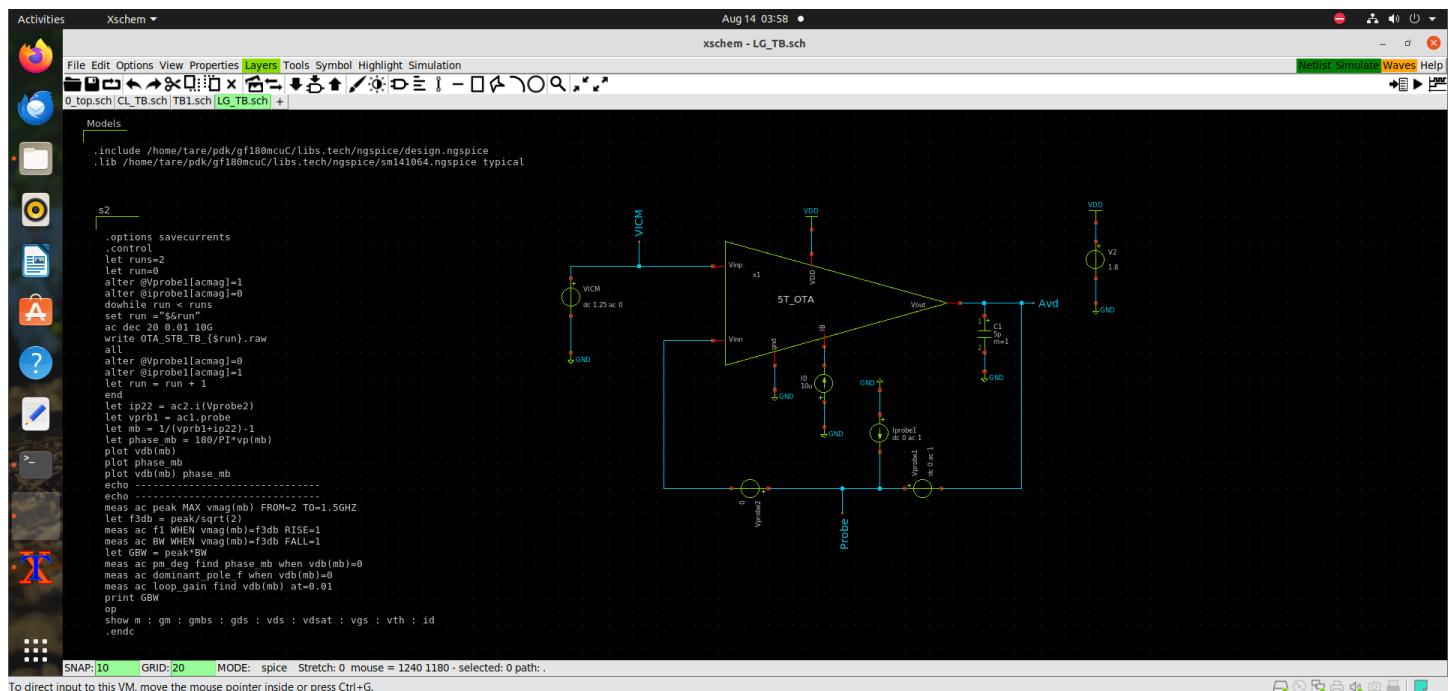
## 2) Loop Gain:

- Put the OTA in a unity gain buffer configuration as shown in the schematic below.
- Use VICM at the middle of the CMIR.



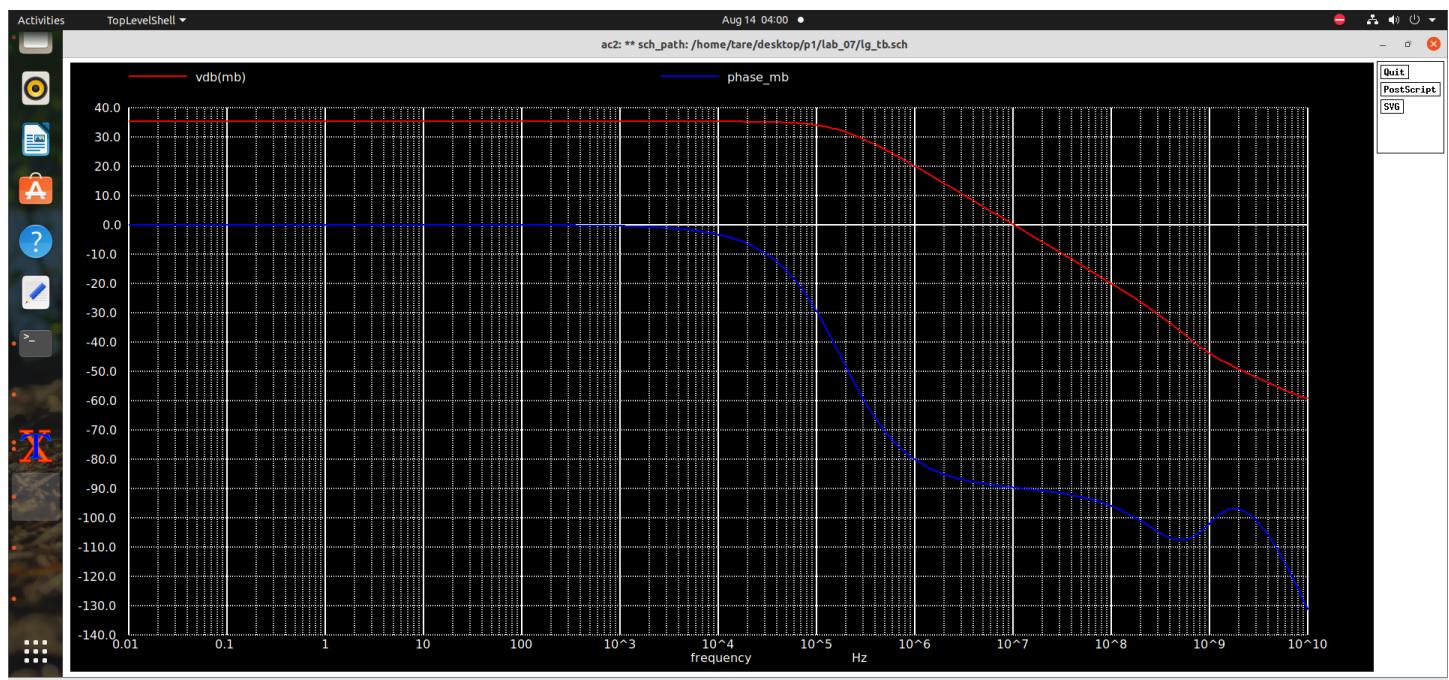- Plot loop gain in dB and phase vs frequency. Show the results in the console.



```

LG_TB.spice" -a || sh
meas ac f1 when vmag(mb)=4.118452e+01 rise=1 failed!
bw = 1.764202e+05
pm_deg = -8.965048e+01
dominant_pole_f = 1.028223e+07
loop_gain = 3.530498e+01
gbw = 1.027537e+07
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000

Note: Starting dynamic gmin stepping
Trying gmin = 1.0000E-03 Note: One successful gmin step
Trying gmin = 1.0000E-04 Note: One successful gmin step
Trying gmin = 1.0000E-05 Note: One successful gmin step
Trying gmin = 1.0000E-06 Note: One successful gmin step
Trying gmin = 1.0000E-07 Note: One successful gmin step
Trying gmin = 1.0000E-08 Note: One successful gmin step
Trying gmin = 1.0000E-09 Note: One successful gmin step
Trying gmin = 1.0000E-10 Note: One successful gmin step
Trying gmin = 1.0000E-11 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Note: Dynamic gmin stepping completed

No. of Data Rows : 1

```

- Compare DC gain and GBW with those obtained from open-loop simulation.

	Open-Loop	Closed-Loop
DC gain	35.43db	35.5db
GBW	10.53MHz	10.3MHz

#### Comment.

- ✓ As  $\beta=1$ , then Loop gain=open loop gain , as we see LG roughly equal the open loop gain .
- ✓ As  $\beta=1$ , then the GBWoL=GBWcL .

- Show the operating point at VICM in the middle of the CMIR.

```

LG_TB.spice" -a || sh
device m_x1.xm6.m0 m_x1.xm5.m0 m_x1.xm4.m0
model nmos_3p3.9 nmos_3p3.13 pmos_3p3.12
gm 0.000119943 0.000465766 0.000201531
gmbs 4.31957e-05 0.000167373 7.83268e-05
gds 7.94782e-07 4.53773e-06 2.39394e-06
vds 0.80185 0.418614 0.916987
vdsat 0.141366 0.139359 0.174148
vgs 0.801854 0.801854 0.916989
vth 0.70816 0.711823 0.7682
id 1e-05 3.85683e-05 1.97552e-05

BSIM4v5: Berkeley Short Channel IGFET Model-4
device m_x1.xm3.m0 m_x1.xm2.m0 m_x1.xm1.m0
model pmos_3p3.12 nmos_3p3.12 nmos_3p3.12
gm 0.000193492 0.000330798 0.000343476
gmbs 7.53668e-05 8.99482e-05 9.34253e-05
gds 2.91135e-06 2.72452e-06 3.39269e-06
vds 0.55599 0.825383 0.464386
vdsat 0.172733 0.086853 0.0891797
vgs 0.916989 0.825384 0.831378
vth 0.770039 0.830396 0.83136
id 1.88131e-05 1.88131e-05 1.97552e-05


ngspice 1 -> 

```


- Compare simulation results (DC gain and GBW) with hand calculations in a table.

✓ DC gain =  $\frac{Acl}{1+LG} = \frac{59.566}{1+59.566} = .9834v/v$

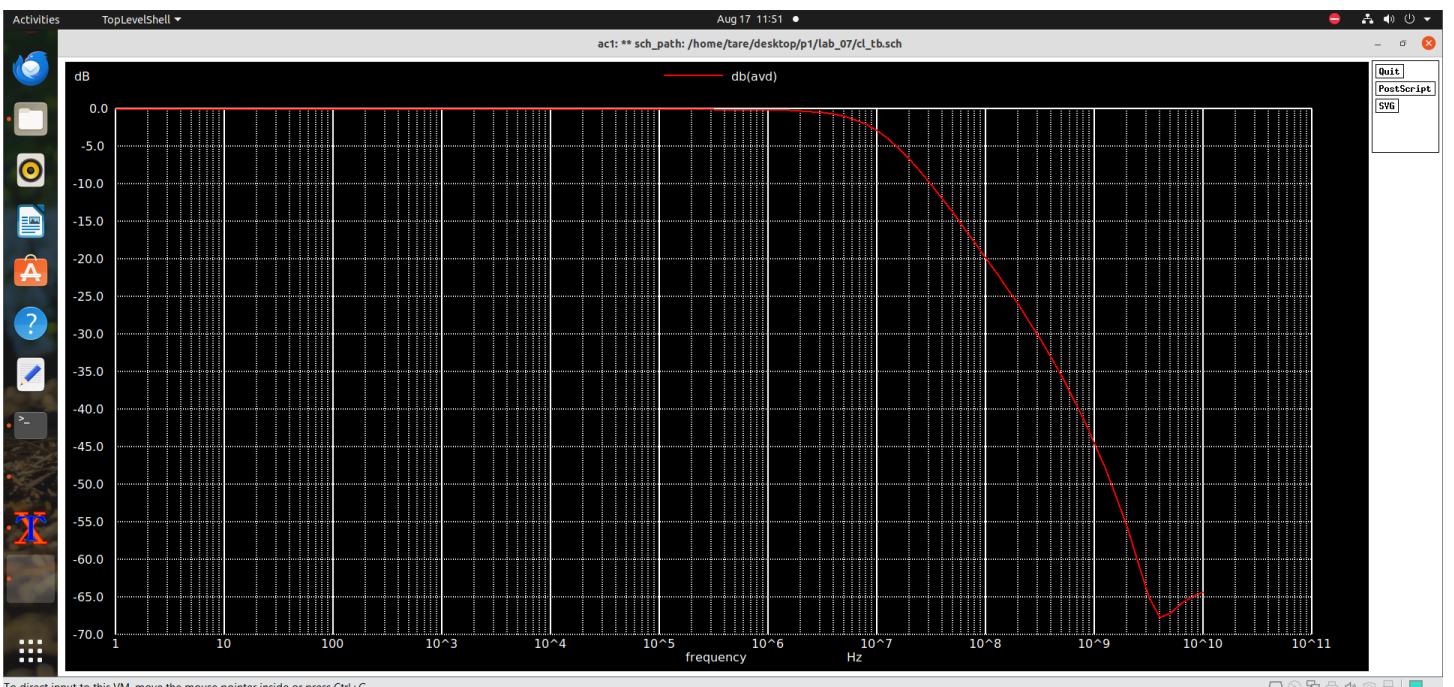✓ GBW =  $\frac{gm1,2}{2\pi CL} = 10.73\text{MHz}$



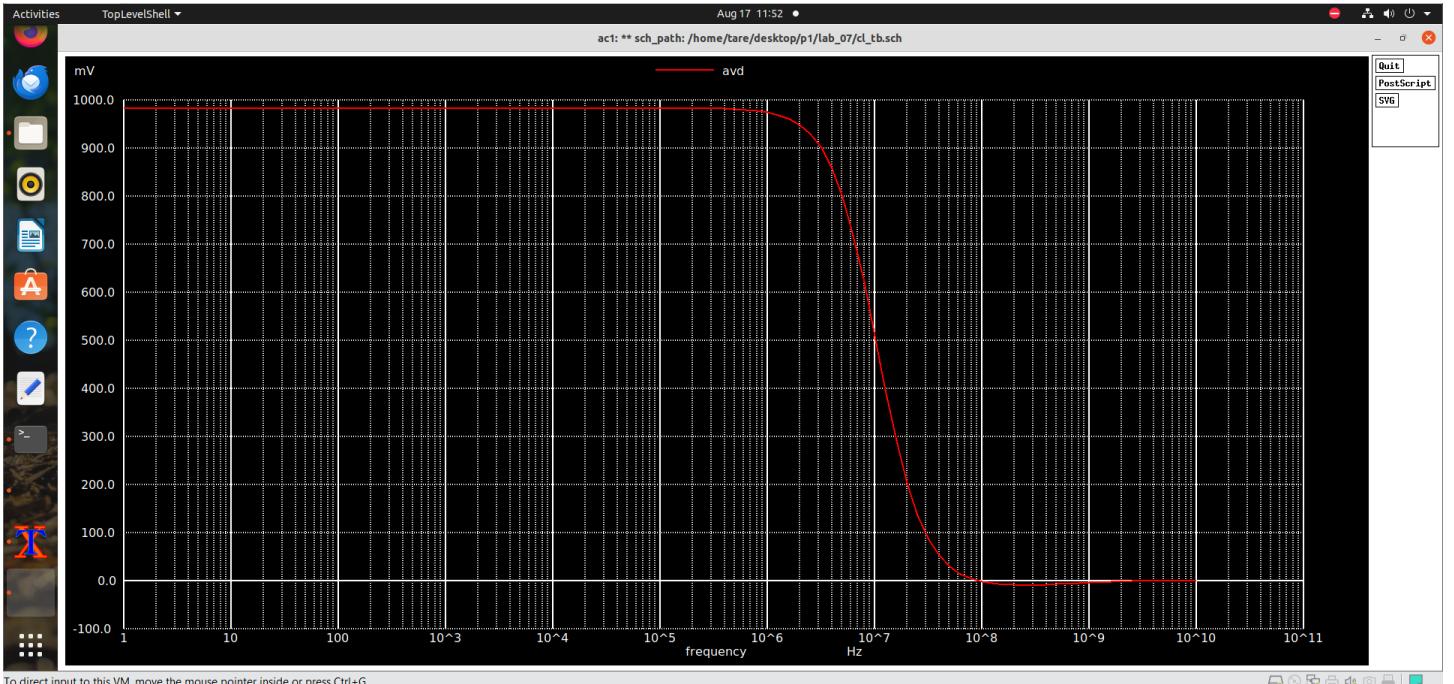To direct input to this VM, move the mouse pointer inside or press Ctrl+G.



To direct input to this VM, move the mouse pointer inside or press Ctrl+G.

```

CL_TB.spice" -a || sh
Circuit: ** sch_path: /home/tare/Desktop/p1/lab_07/cl_tb.sch
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Note: Starting dynamic gmin stepping
Trying gmin = 1.0000E-03 Note: One successful gmin step
Trying gmin = 1.0000E-04 Note: One successful gmin step
Trying gmin = 1.0000E-05 Note: One successful gmin step
Trying gmin = 1.0000E-06 Note: One successful gmin step
Trying gmin = 1.0000E-07 Note: One successful gmin step
Trying gmin = 1.0000E-08 Note: One successful gmin step
Trying gmin = 1.0000E-09 Note: One successful gmin step
Trying gmin = 1.0000E-10 Note: One successful gmin step
Trying gmin = 1.0000E-11 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Note: Dynamic gmin stepping completed
Reference value : 1.00000e+00
No. of Data Rows : 101
peak             = 9.835776e-01 at= 1.000000e+00
peak_db          = -1.438276e-01 at= 1.000000e+00
binary raw file "OTA_TB.raw"
ngspice 1 -> ■

```

```

CL_TB.spice" -a || sh
Doing analysis at TEMP = 27.000000 and TNOM = 27.000000
Note: Starting dynamic gmin stepping
Trying gmin = 1.0000E-03 Note: One successful gmin step
Trying gmin = 1.0000E-04 Note: One successful gmin step
Trying gmin = 1.0000E-05 Note: One successful gmin step
Trying gmin = 1.0000E-06 Note: One successful gmin step
Trying gmin = 1.0000E-07 Note: One successful gmin step
Trying gmin = 1.0000E-08 Note: One successful gmin step
Trying gmin = 1.0000E-09 Note: One successful gmin step
Trying gmin = 1.0000E-10 Note: One successful gmin step
Trying gmin = 1.0000E-11 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Trying gmin = 1.0000E-12 Note: One successful gmin step
Note: Dynamic gmin stepping completed
Reference value : 1.00000e+00
No. of Data Rows : 101
peak             = 9.835776e-01 at= 1.000000e+00
f1               = 1.052691e+07
peak_db          = -1.438276e-01 at= 1.000000e+00
gbw = 1.035403e+07
binary raw file "OTA_TB.raw"
ngspice 1 -> ■

```

	Hand Analysis	Simulation
DC gain	.9834v/v	.984v/v
GBW	10.73MHz	10.35MHz